

# EE 102: INTRODUCTION TO COMPUTER ENGINEERING

## Lecture 3: Combination Logic

4/5/2010

Avinash Kodi, [kodi@ohio.edu](mailto:kodi@ohio.edu)

## Administration


2

- Hw 1 due Wednesday 4/7
- Quiz 1 on Wednesday 4/7 (includes today's lectures)
- Hw 2 will be posted later today
- Lab 1 next week – more information on course webpage
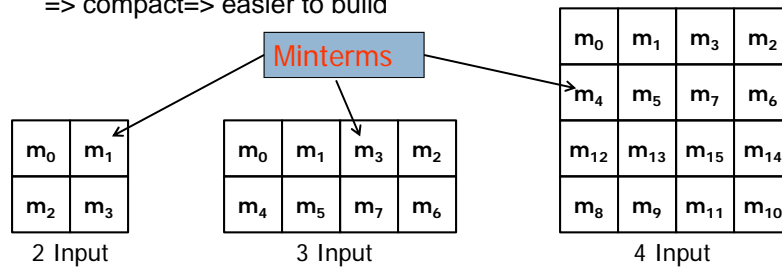
## Karnaugh Maps - Definitions

3

- Specific layouts of truth tables to simplify the logic expressions in Canonical forms to their minimum form
  - ▣ Canonical forms: **SoP (minterms) or PoS (maxterms)**
    - Each min/max term contains all variables => not compact
  - ▣ **The minimum form:** contains the fewest possible terms (operations) and variables (literals)
  - ▣ Can be implemented with fewer logic gates than canonical forms => compact=> easier to build




3 Steps in K-maps: (1) Mapping, (2) Simplification, (3) Reading
 
## Adjacency


4

- Defined by a single variable change in min/max terms
- In K-Maps, each cell is adjacent to the cells that are immediately next to it on any of its 4 sides
  - ▣ **Diagonal neighbors are not adjacent**
  - ▣ **Perimeter cells in any column or row are adjacent (wrap-around adjacency)**
- Useful for reduction:  $m_i + m_{i+1}$  eliminates one variable
  - $AB + A'B = B$
  - $(X+Y)(X+Y') = X$




## Step 1: Mapping a SoP (2 Variables)

5

 


Truth Table


| X | Y | Z = X · Y | Index | Binary |
|---|---|-----------|-------|--------|
| 0 | 0 | 0         | $m_0$ | 00     |
| 0 | 1 | 0         | $m_1$ | 01     |
| 1 | 0 | 0         | $m_2$ | 10     |
| 1 | 1 | 1         | $m_3$ | 11     |

 

 **Step 1c:** place a 1 on the K-map in the cell having the same index



 **Step 1b:** determine the indices of the minterms (or use the variable key on the upper left)



2 Input

**Step 1a:** ensure that each cell of K-map differs by one-bit

## Step 2: SoP Simplification

6

- Objective: to obtain an expression with the least number of terms and literals

- 3 steps in the process of SoP simplification:
  - 2a: **grouping** the 1s in blocks of  $2^n$  adjacent elements:
    - groups of 1,2,4,8,etc.
    - prefer larger groups
    - groups themselves do not have to adjacent
    - each 1 to be included at least in one of the groups
    - groups overlaps (or sharing 1s) allowed
  - 2b: determine the **group product** using adjacency
    - for each group of  $2^n$ ,  $n$  variables are eliminated
  - 2c: **summing** the resulting product terms.


## Step 3: Reading a K-Map

7

### Example


3a: remember to **maximize** groups  
 3b: **decide** carefully which input variable **eliminated** in each group

| X | Y | Z | Index | Binary |
|---|---|---|-------|--------|
| 0 | 0 | 1 | $m_0$ | 00     |
| 0 | 1 | 1 | $m_1$ | 01     |
| 1 | 0 | 0 | $m_2$ | 10     |
| 1 | 1 | 0 | $m_3$ | 11     |

 

## 3-Input K-Maps


8

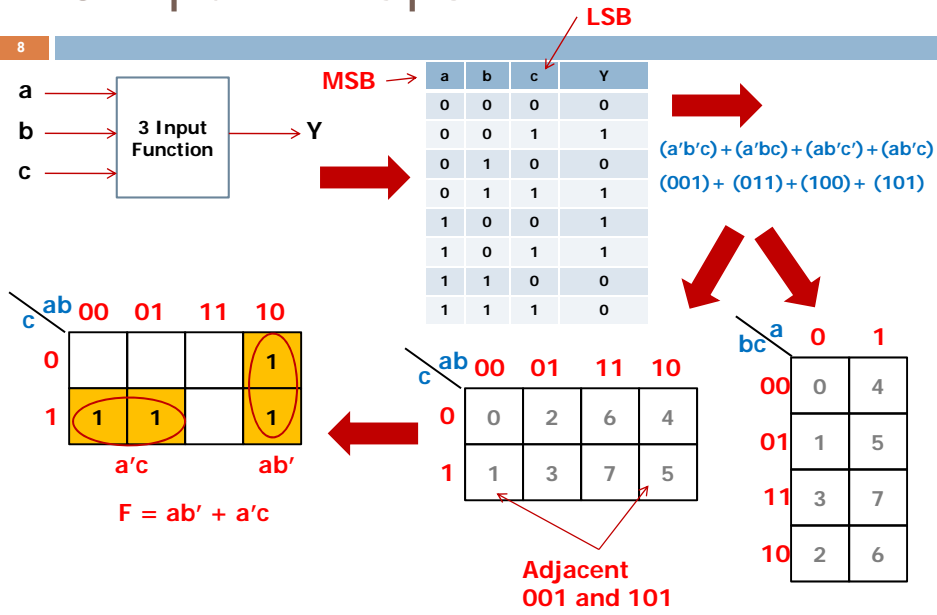

## Example

9

| a | b | c | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

 


$$Y(a,b,c) = a'b + ac'$$
 
## K-Maps: PoS Form

10

- In case of PoS => group and reduce zeros (0)
  - Corresponding to maxterms
  - Should give the same function as SoP



$$Y(a,b,c) = a'b + ac' \quad \text{SoP}$$


$$Y(A, B, C) = (a + b)(a' + c') \quad \text{PoS}$$

$$Y = aa' + ac' + a'b + bc' \\ = ac' + a'b \quad (\text{Consensus})$$
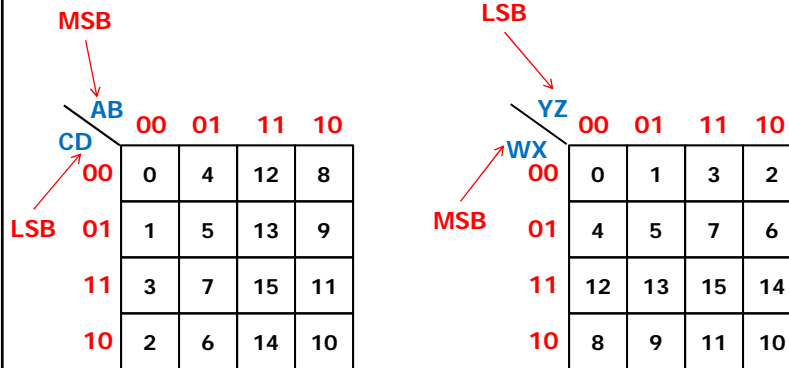
## 4-Variable K-Maps

11


- Each term composed of 4 variables
- Similar to and expansion of 3-variable tables


 
## Example

12


$$F(a,b,c,d) = \sum(0,2,4,5,6,7,8,10,11,12,14,15)$$



$$F(a,b,c,d) = a'b + ac + d'$$

# Examples of Combining

13

 


# More Examples


14

$$F(a,b,c,d) = \Sigma(1,3,4,5,19,12,13)$$
 
$$F(a,b,c,d) = \Sigma(0,2,3,5,6,7,8,10,11,14,15)$$


 
$$f_1 = \Sigma m(1, 3, 4, 5, 10, 12, 13) = bc' + a'b'd + ab'cd'$$



$$f_2 = \Sigma m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15) = c + b'd' + a'bd$$

## Essential and Non-Essential Prime Implicants

15

- A product term is an **implicant** of a function, if the function has the value of 1 for all minterms
- If the removal of any literal from an implicant P results in a product term that is not an implicant of the function, then P is a **prime implicant**
- If the minterm of a function is included in only one prime implicant, that prime implicant is **essential**

## Essential and Non-Essential Prime Implicants

16

$$F(a,b,c,d) = \sum(1,3,4,5,6,7,12,14)$$

|    |    | AB |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| CD | 00 |    | 1  | 1  |    |
|    | 01 | 1  | 1  |    |    |
|    | 11 | 1  | 1  |    |    |
|    | 10 |    | 1  | 1  |    |

$A'B$ 
 $BD'$

Prime Implicants =  $A'D$ ,  $A'B$  and  $BD'$

Essential Prime Implicants =  $A'D + BD'$

Non-essential Prime Implicant =  $A'B$



## Essential and Non-Essential Prime Implicants


17

$$F(a,b,c,d) = \sum(0, 5, 10, 11, 12, 13, 15)$$
 
## Combinational Circuits

18

- System of interconnected logic gates whose outputs **at any time** are determined by combining the values of the applied **inputs only**
  - ▣ Performs an operation specified by a set of Boolean expressions
  - ▣ Consists of input variables, output variables, logic gates and interconnections



- ▣ Examples: **Encoders, Decoders, Multiplexers, Demultiplexers, Adders, Comparators**

## Design Procedure


19

- The design starts from the specification of the problem and culminates in a logic diagram or set of Boolean equations. The procedure involves the following steps:
  1. Using the specifications of the circuit, **determine the input and output variables.**
  2. **Derive the truth table** that defines the required relationship between inputs and outputs.
  3. **Break the circuit into small single-output blocks.**
  4. **Obtain the simplified Boolean functions** for each output in terms of input variables
  5. **Draw the logic diagram.**
  6. **Verify the design** (logic simulation).

## Example 1: Code Converter (1/2)

20

| Decimal | Input BCD |   |   |   | Output Excess-3 |   |   |   |
|---------|-----------|---|---|---|-----------------|---|---|---|
|         | A         | B | C | D | W               | X | Y | Z |
| 0       | 0         | 0 | 0 | 0 | 0               | 0 | 1 | 1 |
| 1       | 0         | 0 | 0 | 1 | 0               | 1 | 0 | 0 |
| 2       | 0         | 0 | 1 | 0 | 0               | 1 | 0 | 1 |
| 3       | 0         | 0 | 1 | 1 | 0               | 1 | 1 | 0 |
| 4       | 0         | 1 | 0 | 0 | 0               | 1 | 1 | 1 |
| 5       | 0         | 1 | 0 | 1 | 1               | 0 | 0 | 0 |
| 6       | 0         | 1 | 1 | 0 | 1               | 0 | 0 | 1 |
| 7       | 0         | 1 | 1 | 1 | 1               | 0 | 1 | 0 |
| 8       | 1         | 0 | 0 | 0 | 1               | 0 | 1 | 1 |
| 9       | 1         | 0 | 0 | 1 | 1               | 1 | 0 | 0 |

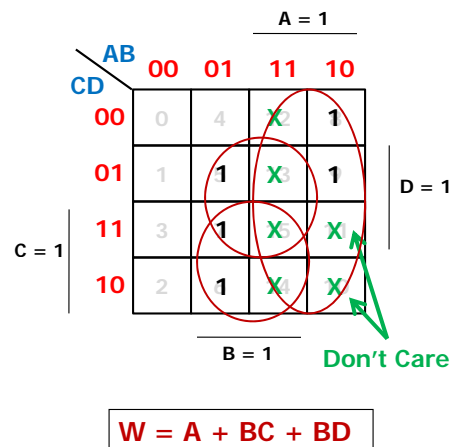

## Example 1: Code Converter (2/2)

21

|       |    |       |    |    |    |    |
|-------|----|-------|----|----|----|----|
|       |    | A = 1 |    |    |    |    |
|       |    | AB    | 00 | 01 | 11 | 10 |
| C = 1 | CD | 00    | 0  | 1  | X  | 8  |
|       | 01 | 1     | 5  | X  | 1  |    |
|       | 11 | 1     | 7  | X  | X  |    |
|       | 10 | 1     | 6  | X  | X  |    |
|       |    | B = 1 |    |    |    |    |

$X = BC'D' + B'D + B'C$

|       |    |       |    |    |    |    |
|-------|----|-------|----|----|----|----|
|       |    | A = 1 |    |    |    |    |
|       |    | AB    | 00 | 01 | 11 | 10 |
| C = 1 | CD | 00    | 1  | 1  | X  | 1  |
|       | 01 | 1     | 5  | X  | 9  |    |
|       | 11 | 1     | 1  | X  | X  |    |
|       | 10 | 2     | 6  | X  | X  |    |
|       |    | B = 1 |    |    |    |    |

$Y = C'D' + CD$

$Z = D'$

## Example Code Converter: Circuit Design


22

$W = A + BC + BD = A + B(C + D)$

$X = BC'D' + B'D + B'C = BC'D' + B'(C + D)$

$Y = C'D' + CD$

$Z = D'$

 

## Example 2

23

Truth Table for BCD-to-Seven-Segment Decoder

| BCD Input        |   |   |   | Seven-Segment Decoder |   |   |   |   |   |   |
|------------------|---|---|---|-----------------------|---|---|---|---|---|---|
| A                | B | C | D | a                     | b | c | d | e | f | g |
| 0                | 0 | 0 | 0 | 1                     | 1 | 1 | 1 | 1 | 1 | 0 |
| 0                | 0 | 0 | 1 | 0                     | 1 | 1 | 0 | 0 | 0 | 0 |
| 0                | 0 | 1 | 0 | 1                     | 1 | 0 | 1 | 1 | 0 | 1 |
| 0                | 0 | 1 | 1 | 1                     | 1 | 1 | 1 | 0 | 0 | 1 |
| 0                | 1 | 0 | 0 | 0                     | 1 | 1 | 0 | 0 | 1 | 1 |
| 0                | 1 | 0 | 1 | 1                     | 0 | 1 | 1 | 0 | 1 | 1 |
| 0                | 1 | 1 | 0 | 1                     | 0 | 1 | 1 | 1 | 1 | 1 |
| 0                | 1 | 1 | 1 | 1                     | 1 | 1 | 0 | 0 | 0 | 0 |
| 1                | 0 | 0 | 0 | 1                     | 1 | 1 | 1 | 1 | 1 | 1 |
| 1                | 0 | 0 | 1 | 1                     | 1 | 1 | 1 | 0 | 1 | 1 |
| All other inputs |   |   |   | 0                     | 0 | 0 | 0 | 0 | 0 | 0 |



(a) Segment designation



(b) Numeric designation for display

$$a = \overline{AC} + \overline{ABD} + \overline{BCD} + \overline{ABC}$$

$$b = \overline{AB} + \overline{ACD} + \overline{ACD} + \overline{ABC}$$

$$c = \overline{AB} + \overline{AD} + \overline{BCD} + \overline{ABC}$$

$$d = \overline{ACD} + \overline{ABC} + \overline{BCD} + \overline{ABC} + \overline{ABCD}$$

$$e = \overline{ACD} + \overline{BCD}$$

$$f = \overline{ABC} + \overline{ACD} + \overline{ABD} + \overline{ABC}$$

$$g = \overline{ACD} + \overline{ABC} + \overline{ABC} + \overline{ABC}$$

7 output functions

## Positive and Negative Representations

| Code | Signed Magnitude | One's Complement | Two's Complement |
|------|------------------|------------------|------------------|
| 000  | +0               | +0               | +0               |
| 001  | +1               | +1               | +1               |
| 010  | +2               | +2               | +2               |
| 011  | +3               | +3               | +3               |
| 100  | -0               | -3               | -4               |
| 101  | -1               | -2               | -3               |
| 110  | -2               | -1               | -2               |
| 111  | -3               | -0               | -1               |

- Issues: balance, number of zeros, ease of operation
- Which one is best? Why?

## 1's Complement

25

- 1's complement: Convert all 0 to 1 and 1 to 0 (invert all bits)

| Number | 1's Complement |
|--------|----------------|
| +7     | 00111          |
| -7     | 11000          |

$$(7)_{10} = 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = 00111$$

1's Complement    11000

                                  ↑  
Not a sign bit

## 1's Complement

26

- Representing **negative numbers** for  $n = 32$  bits
  - $(b_{31} \times -2^{31}) + (b_{30} \times 2^{30}) + (b_{29} \times 2^{29}) + \dots + (b_1 \times 2^1) + (b_0 \times 2^0) + 1$
- Example: if  $n = 4$  bits, decimal value of 1000
  - $(1 \times -2^3) + (0 \times 2^2) + (0 \times 2^1) + (0 \times 2^0) + 1 = -7$
  - Easier method is to convert into positive number and then determine the decimal equivalent

## 2's Complement

27

- Invert all the bits and ADD 1

| Original Number | 1's Complement | 2's Complement |
|-----------------|----------------|----------------|
| +7              | 0000111        | 0000111        |
| -7              | 11111000       | 11111001       |

$$\begin{array}{r}
 \text{1's} \quad 11111000 \\
 + \quad \quad \quad 1 \\
 \hline
 \text{2's} \quad 11111001
 \end{array}$$

### Other method

Start at the right and complement all bits to the left of the first 1.

$$\begin{array}{c}
 \boxed{000011} \quad 1 \quad \xrightarrow{\text{2's}} \quad 11111001 \\
 \text{2's}
 \end{array}$$

## 2's Complement

- Representing **positive and negative numbers** for  $n = 32$  bits
  - $(b_{31} \times -2^{31}) + (b_{30} \times 2^{30}) + (b_{29} \times 2^{29}) + \dots + (b_1 \times 2^1) + (b_0 \times 2^0)$
- Example: if  $n = 4$  bits, decimal value of 1000
  - $(1 \times -2^3) + (0 \times 2^2) + (0 \times 2^1) + (0 \times 2^0) = -8$

## Number Representation for 4 Bits

| Binary | 1's Complement | 2's Complement | Unsigned Decimal |
|--------|----------------|----------------|------------------|
| 1000   | -7             | -8             | 8                |
| 1001   | -6             | -7             | 9                |
| 1010   | -5             | -6             | 10               |
| 1011   | -4             | -5             | 11               |
| 1100   | -3             | -4             | 12               |
| 1101   | -2             | -3             | 13               |
| 1110   | -1             | -2             | 14               |
| 1111   | -0             | -1             | 15               |
| 0000   | +0             | 0              | 0                |
| 0001   | +1             | +1             | 1                |
| 0010   | +2             | +2             | 2                |
| 0011   | +3             | +3             | 3                |
| 0100   | +4             | +4             | 4                |
| 0101   | +5             | +5             | 5                |
| 0110   | +6             | +6             | 6                |
| 0111   | +7             | +7             | 7                |

## 1's Complement Operations

30

- Example: if  $n = 8$ , add  $-11$  and  $-20$ 
  - $+11 = 00001011$  and  $+20 = 00010100$
  - Bit-by-bit complement
  - $-11 = 11110100$  and  $-20 = 11101011$

$$\begin{array}{r}
 \begin{array}{cccccccc}
 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 \\
 \swarrow & \swarrow & \swarrow & \swarrow & \swarrow & \swarrow & \swarrow & \swarrow \\
 1 & 1 & 1 & 1 & 1 & 0 & 1 & 0 & 0 & 0 \\
 + & & & & & & & & & \\
 \hline
 1 & 1 & 0 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \\
 \hline
 & & & & & & & & & 1 \\
 + & & & & & & & & & \\
 \hline
 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0
 \end{array}
 \end{array}
 \begin{array}{l}
 -11 \\
 -20 \\
 \\
 -31
 \end{array}$$

Must add the carry-out 1 to the result to get the correct answer

## More 1's Complement Operations

31

- Addition of two negative numbers, n= 4 add -5 and -6

|   |   |   |   |   |    |
|---|---|---|---|---|----|
|   | 1 | 0 | 0 | 0 |    |
| + | 1 | 1 | 0 | 0 | -6 |
| + | 1 | 0 | 1 | 0 | -5 |
|   | 0 | 0 | 1 | 1 |    |
|   | 0 | 1 | 0 | 0 | +4 |

Wrong answer because of carry addition (OVERFLOW)

## 2's Complement Operations

32

- Example: Add -8 and +19 in 2's Complement for n = 8 bits
  - ▣ +8 = 00001000, 2's Complement = 11111000
  - ▣ +19 = 00010011

|   |   |   |   |   |   |   |   |   |     |
|---|---|---|---|---|---|---|---|---|-----|
|   | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |     |
| + | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | -8  |
| + | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | +19 |
|   | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | +11 |



Discard the carry-out 1 in 2's complement

2's Complement subtraction can be handled by a summation i.e.  
 $A - B = A + B' + 1$


  
## Overflow

- Overflow: the result is too large to represent in 4 bits
- Overflow occurs when
  - ▣ adding two positives yields a negative
  - ▣ or, adding two negatives gives a positive
  - ▣ or, subtract a negative from a positive gives a negative
  - ▣ or, subtract a positive from a negative gives a positive
- On your own: **Prove** you can detect overflow by:




## Adders

34

- Half-Adder

| Inputs |   | Outputs |   |
|--------|---|---------|---|
| X      | Y | C       | S |
| 0      | 0 | 0       | 0 |
| 1      | 0 | 0       | 1 |
| 0      | 1 | 0       | 1 |
| 1      | 1 | 1       | 0 |
 
$$\begin{aligned}
 C &= XY \\
 S &= XY' + X'Y \\
 &= X \oplus Y
 \end{aligned}$$



## Full Adders

35

| Inputs |   |                 | Outputs          |            |
|--------|---|-----------------|------------------|------------|
| X      | Y | Z<br>(Carry-In) | C<br>(Carry-Out) | S<br>(Sum) |
| 0      | 0 | 0               | 0                | 0          |
| 0      | 0 | 1               | 0                | 1          |
| 0      | 1 | 0               | 0                | 1          |
| 0      | 1 | 1               | 1                | 0          |
| 1      | 0 | 0               | 0                | 1          |
| 1      | 0 | 1               | 1                | 0          |
| 1      | 1 | 0               | 1                | 0          |
| 1      | 1 | 1               | 1                | 1          |

Carry-in bit (Z) takes into account any carry information coming from earlier stages of a multi-bit addition

## Full Adders

36

|   |   | $Z = 1$ |    |    |    |    |
|---|---|---------|----|----|----|----|
|   |   | YZ      | 00 | 01 | 11 | 10 |
| X | 0 |         | 1  |    | 1  |    |
|   | 1 | 1       |    | 1  |    |    |
|   |   | $Y = 1$ |    |    |    |    |

$$S = XYZ + X'YZ' + XY'Z' + X'Y'Z$$

$$= X \oplus Y \oplus Z$$

|   |   | $Z = 1$ |    |    |    |    |
|---|---|---------|----|----|----|----|
|   |   | YZ      | 00 | 01 | 11 | 10 |
| X | 0 |         |    | 1  |    |    |
|   | 1 |         | 1  | 1  | 1  |    |
|   |   | $Y = 1$ |    |    |    |    |

$$C = XY + YZ + XZ$$

$$= XY + Z(X + Y)$$

(equivalent)

$$= XY + Z(XY' + X'Y)$$


$$= XY + Z(X \oplus Y)$$

# Full Adders

37

$$S = X \oplus Y \oplus Z$$



$$C = XY + Z(X \oplus Y)$$

 

Using the common XOR terms, a single full adder can be realized using two half adders and an additional OR gate. Outputs are the sum (S) and carry-out (C)

# Multi-Bit Full Adder (Ripple Carry Adder)


38

  

□ Ripple adder produces the arithmetic sum of two binary numbers using no memory elements:

- **Slow:** note that one must wait until all carries propagate to next stage and  $C_{out}$  emerges

## Issues with Ripple Adder

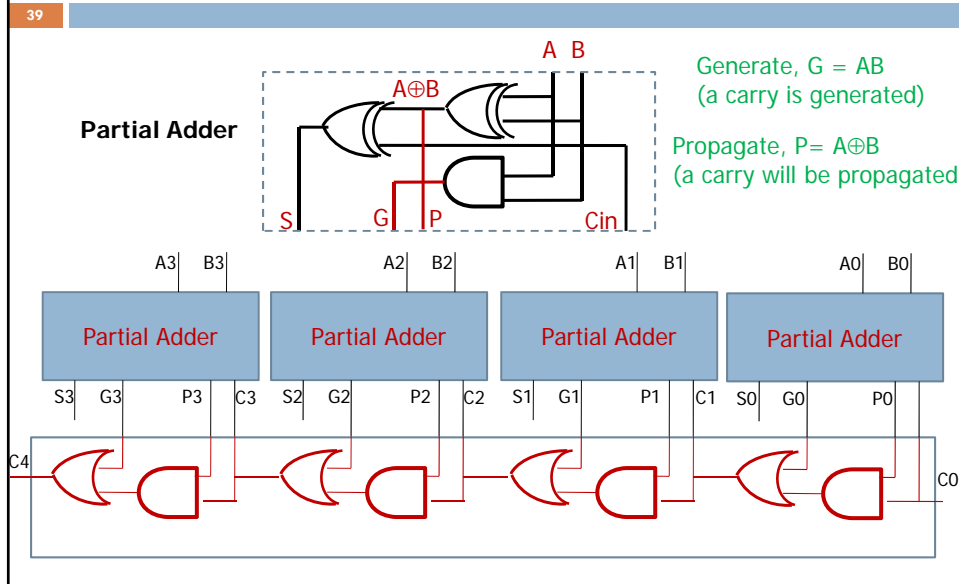

## Carry Look-Ahead (CLA) Adder

40


- $c_{i+1} = c_i (b_i \oplus a_i) + (a_i \cdot b_i)$
- $c_1 = (a_0 \cdot b_0) + (a_0 \oplus b_0) \cdot c_0$
- $c_2 = (a_1 \cdot b_1) + (a_1 \oplus b_1) \cdot c_1$   
 $= (a_1 \cdot b_1) + (a_1 \oplus b_1) ((a_0 \cdot b_0) + (a_0 \oplus b_0) \cdot c_0)$
- Repeated use of  $(a_i \cdot b_i)$  and  $(a_i \oplus b_i)$  in the formula
- **Generate ( $g_i$ ) and Propagate ( $p_i$ )**
- $g_i = a_i \cdot b_i$  [a carry is always generated]
- $p_i = a_i \oplus b_i$  [if  $(i-1)^{\text{th}}$  bit has a carry, it will be propagated to  $(i+1)^{\text{th}}$  bit]
- $c_{i+1} = g_i + p_i \cdot c_i$

The carry terms are faster because they are evaluated by the knowledge of the  $p_i$  and  $g_i$  terms from preceding stages:  
More expensive to build
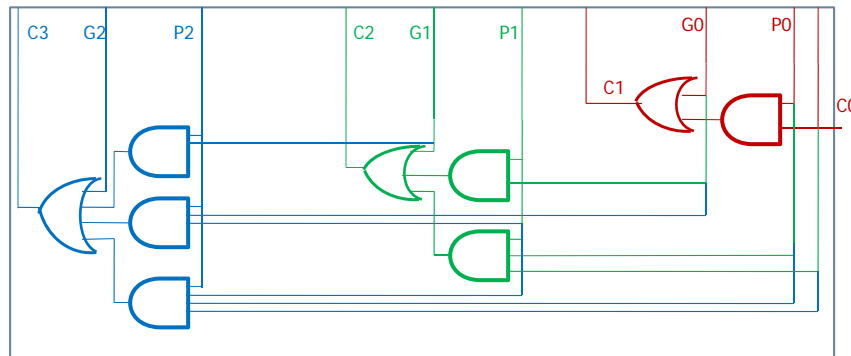
# Carry Look Ahead

41


- $c1 = g0 + p0.c0$
- $c2 = g1 + p1.c1 = g1 + p1.(g0 + p0.c0) = g1 + p1.g0 + p1.p0.c0$
- $c3 = g2 + p2.c2 = g2 + p2.(g1 + p1.g0 + p1.p0.c0) = g2 + p2.g1 + p2.p1.g0 + p2.p1.p0.c0$


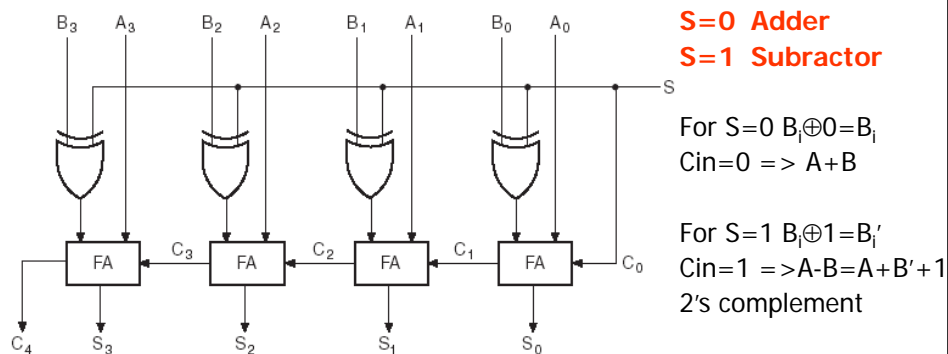
# Binary Adder-Subtractors

42

- Design a 4-bit binary adder and subtractor using a Full Adders depending on the select logic,
  - $S = 0$  implies addition and  $S = 1$  implies subtraction
  - Hint:  $A - B = A + B' + 1$



# Multiplexers


43

- A combinational circuit that selects binary information from one of many input lines and directs the information to a single output line
  - ▣ Select input variables to decide the output
  - ▣ Example: 4-to-1 Mux (Multiplexer)
    - 4 inputs (D0, D1, D2, D3)
    - 1 output Y
    - Mux Selector Logic (S0, S1)

| S0 | S1 | Y  |
|----|----|----|
| 0  | 0  | D0 |
| 1  | 0  | D1 |
| 0  | 1  | D2 |
| 1  | 1  | D3 |


## 4-to-1 Multiplexer

44

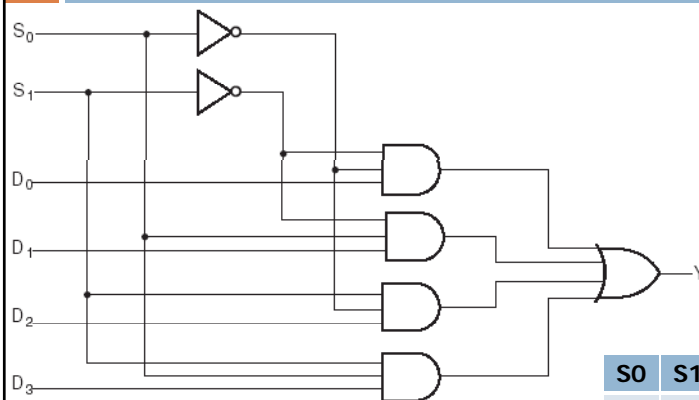

| S0 | S1 | Y  |
|----|----|----|
| 0  | 0  | D0 |
| 1  | 0  | D1 |
| 0  | 1  | D2 |
| 1  | 1  | D3 |


# Multiplexer Example - 1

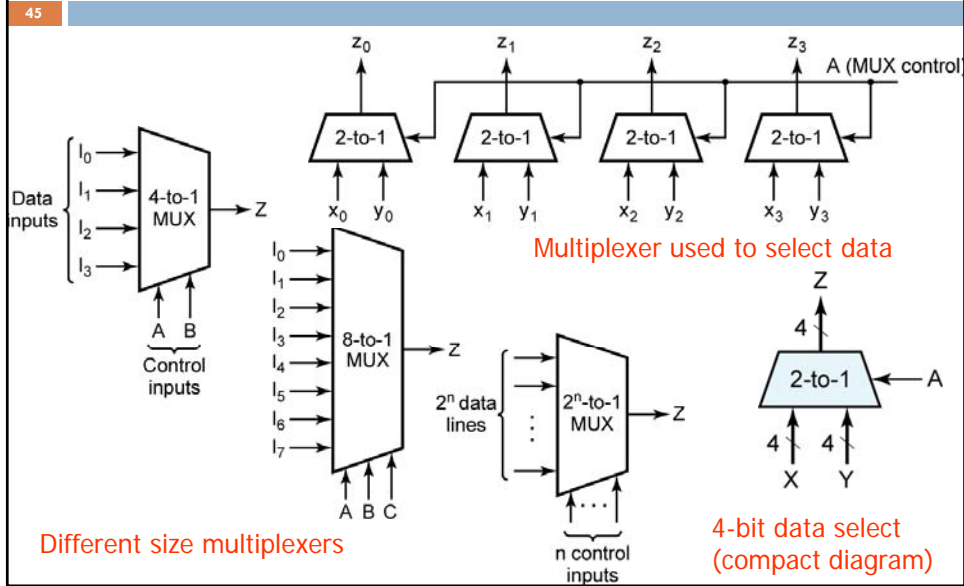

# Multiplexer Example - 3

- 46
- Multiplexers maybe used to manipulate/design other functions
    - Especially useful to re-use/expand large blocks

| X | Y | Z | F | Select Conditions |
|---|---|---|---|-------------------|
| 0 | 0 | 0 | 0 | $F = Z$           |
| 0 | 0 | 1 | 1 |                   |
| 0 | 1 | 0 | 1 | $F = \bar{Z}$     |
| 0 | 1 | 1 | 0 |                   |
| 1 | 0 | 0 | 0 | $F = 0$           |
| 1 | 0 | 1 | 0 |                   |
| 1 | 1 | 0 | 1 | $F = 1$           |
| 1 | 1 | 1 | 1 |                   |

 


Block Diagram

## Multiplexer Example - 4

47

$$F(A, B, C, D) = \sum m(1,3,4,11,12,13,14,15)$$


| A | B | C | D | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

 
 
## Three-State Buffers

48

- A gate output can be connected to limited number of input devices
- A buffer can increase the driving capability of a gate output






# Comparators

49


- Compares the magnitude of two quantities to determine the relationship between them
- In its simplest form, a comparator circuit determines whether two numbers are equal

### Basic comparator operations

 
 
### Example

Logic diagram for comparison of two 2-bit binary numbers




# Design Problem: Comparators

50

Compare two four bit numbers and indicate when A=B and when A>B.

To determine an inequality of numbers A and B, first examine the highest-order bit in each number. The following conditions are possible:

 - If A<sub>3</sub>=1 and B<sub>3</sub>=0 number A is greater than B
- If A<sub>3</sub>=0 and B<sub>3</sub>=1 number A is less than number B
- If A<sub>3</sub>=B<sub>3</sub> then examine the next lower bit position for an inequality



# Decoders

51

- Combinational circuits that converts binary information from n coded inputs to a maximum of 2<sup>n</sup> unique outputs

| Inputs |    |    | Outputs |    |    |    |    |    |    |    |
|--------|----|----|---------|----|----|----|----|----|----|----|
| A2     | A1 | A0 | D7      | D6 | D5 | D4 | D3 | D2 | D1 | D0 |
| 0      | 0  | 0  | 0       | 0  | 0  | 0  | 0  | 0  | 0  | 1  |
| 0      | 0  | 1  | 0       | 0  | 0  | 0  | 0  | 0  | 1  | 0  |
| 0      | 1  | 0  | 0       | 0  | 0  | 0  | 0  | 1  | 0  | 0  |
| 0      | 1  | 1  | 0       | 0  | 0  | 0  | 1  | 0  | 0  | 0  |
| 1      | 0  | 0  | 0       | 0  | 0  | 1  | 0  | 0  | 0  | 0  |
| 1      | 0  | 1  | 0       | 0  | 1  | 0  | 0  | 0  | 0  | 0  |
| 1      | 1  | 0  | 0       | 1  | 0  | 0  | 0  | 0  | 0  | 0  |
| 1      | 1  | 1  | 1       | 0  | 0  | 0  | 0  | 0  | 0  | 0  |

$$D_0 = \overline{A_2} \overline{A_1} \overline{A_0}$$

$$D_1 = \overline{A_2} \overline{A_1} A_0$$

$$D_2 = \overline{A_2} A_1 \overline{A_0}$$

$$D_3 = \overline{A_2} A_1 A_0$$

$$D_4 = A_2 \overline{A_1} \overline{A_0}$$


$$D_5 = A_2 \overline{A_1} A_0$$

$$D_6 = A_2 A_1 \overline{A_0}$$

$$D_7 = A_2 A_1 A_0$$

# Decoder (3-to-8)

52

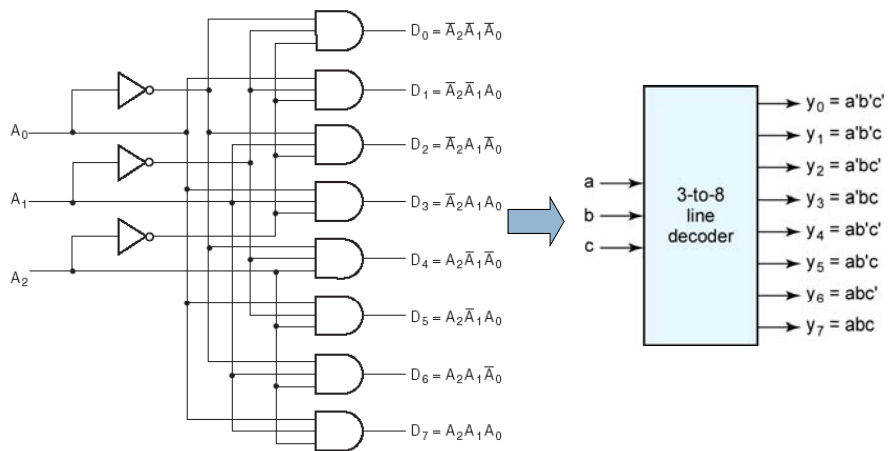


3-to-8-line decoder
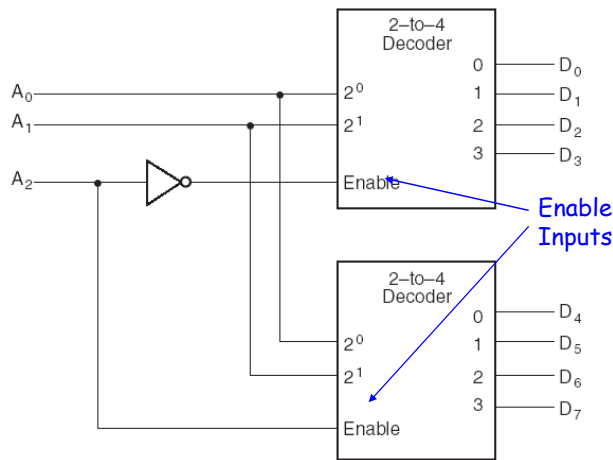
# Decoder Expansions

53


- 3-to-8-line decoder from 2-to-4-line decoders with ENABLE



# 4-to-10 BCD to Decimal Decoder

54

| Input BCD |   |   |   | Output Decimal |   |   |   |   |   |   |   |   |   |
|-----------|---|---|---|----------------|---|---|---|---|---|---|---|---|---|
| A         | B | C | D | 0              | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 |
| 0         | 0 | 0 | 0 | 0              | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0         | 0 | 0 | 1 | 1              | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0         | 0 | 1 | 0 | 1              | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0         | 0 | 1 | 1 | 1              | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0         | 1 | 0 | 0 | 1              | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0         | 1 | 0 | 1 | 1              | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0         | 1 | 1 | 0 | 1              | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 0         | 1 | 1 | 1 | 1              | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1         | 0 | 0 | 0 | 1              | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1         | 0 | 0 | 1 | 1              | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1         | 0 | 1 | 0 | 1              | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

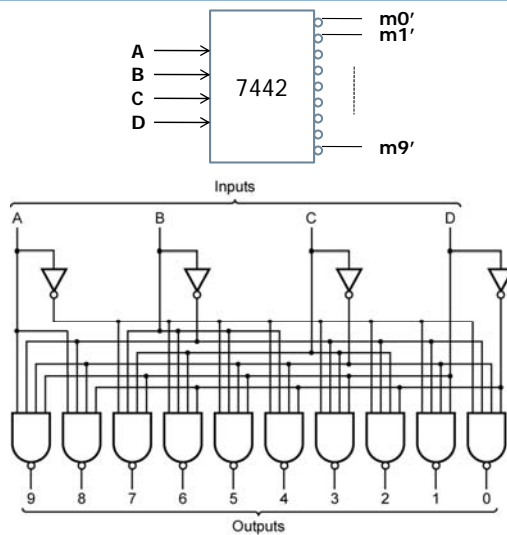


(a) Logic diagram
 
# Programmable Logic Devices

55

- PLD can be programmed to provide a variety of different logic functions
- A PLA has  $n$  inputs and  $m$  outputs, can realize  $m$  functions of  $n$  variables using a AND array and OR array



# Designing PLD

56

$$F_0 = A'B' + AC'$$

$$F_1 = AC' + B$$

$$F_2 = A'B' + BC'$$

$$F_3 = B + AC$$

| Product Term | Inputs |    |    | Outputs        |                |                |                |
|--------------|--------|----|----|----------------|----------------|----------------|----------------|
|              | A      | B  | C  | F <sub>0</sub> | F <sub>1</sub> | F <sub>2</sub> | F <sub>3</sub> |
| A'B'         | 0      | 0  | -- | 1              | 0              | 1              | 0              |
| AC'          | 1      | -- | 0  | 1              | 1              | 0              | 0              |
| B            | --     | 1  | -- | 0              | 1              | 0              | 1              |
| BC'          | --     | 1  | 0  | 0              | 0              | 1              | 0              |
| AC           | 1      | -- | 1  | 0              | 0              | 0              | 1              |