

EE 224: INTRODUCTION TO DIGITAL CIRCUITS & COMPUTER DESIGN

Lecture 4: Sequential Logic – 1 Latches & Flip Flops


4/19/2010

Avinash Kodi, kodi@ohio.edu

Introduction to Sequential Logic

2

 - In sequential logic circuits the output depends not only on the present input but also on the past sequence of inputs. Thus, these circuits must **'remember'** the past history of the inputs to evaluate the present output.




- **Latches** and **flip-flops (FF)** are commonly used storage (memory) elements in sequential circuits. Basically, latches and FFs have one or more inputs that can cause the output state to assume one of the two binary levels.

Basic Concepts

3


- In sequential logic, time must be divided to specific units/intervals to order the output events or states. According to times at which the inputs are evaluated and output state changes, they may be called
 - **Synchronous sequential circuits:** all inputs ready and outputs are evaluated at discrete instants of time dictated by the clock signal (pulses).
 - **Asynchronous sequential circuit:** the inputs arrive at different times and outputs evaluated continuously

 

Feedback and Timing

4


- **Feedback:** output is fed into input to impact the circuit's (next) output. 'Next' is the following clock pulse in **synchronous** circuits and as soon as the input is available (stable) in **asynchronous** circuits
 - **Stability:** The feedback can create unstable conditions
- **Timing:** Delays (time need for output evaluation) between input and outputs are important in sequential logic circuits.

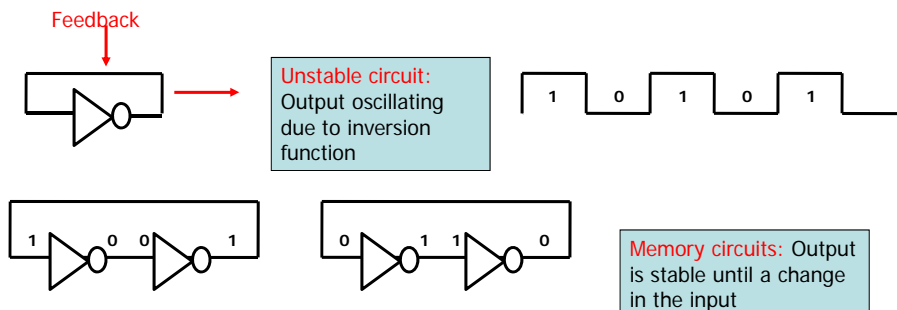

Latches – SR Latch

5

 
- A storage element can maintain a binary state indefinitely (as long as power is ON) or until inputs change. The most basic storage elements are latches, from which more complex FFs are usually constructed.
- The simplest latch is a tri-stable **Set-Reset (SR)** circuit built from two **NOR gates** in cross feedback





SR Latch

6

 - Set=1 and R=0 ⇒ SETs the Q (1) output and RESETs Q' (0) (**Write**)
- Set=0 and R=1 ⇒ RESETs the Q output (0) and SETs Q' (1) (**Erase**)
- Set=0 and R=0 ⇒ Retains the states of Q and Q' (**No change: Storage**)
- Set=1 and R=1 ⇒ invalid or forbidden state Q=Q'=0! (No use)




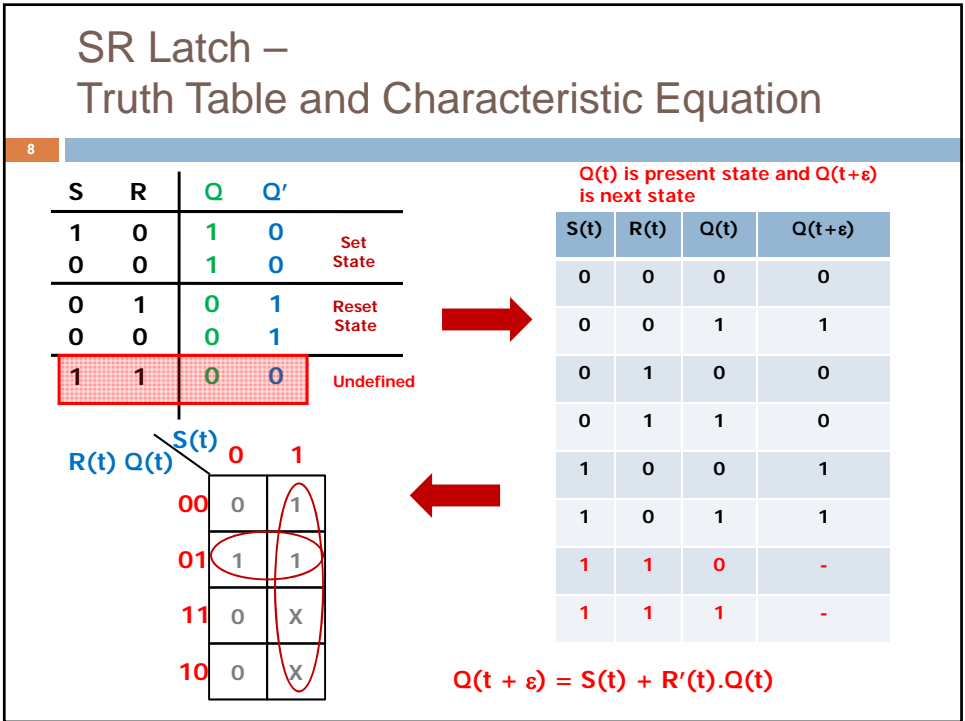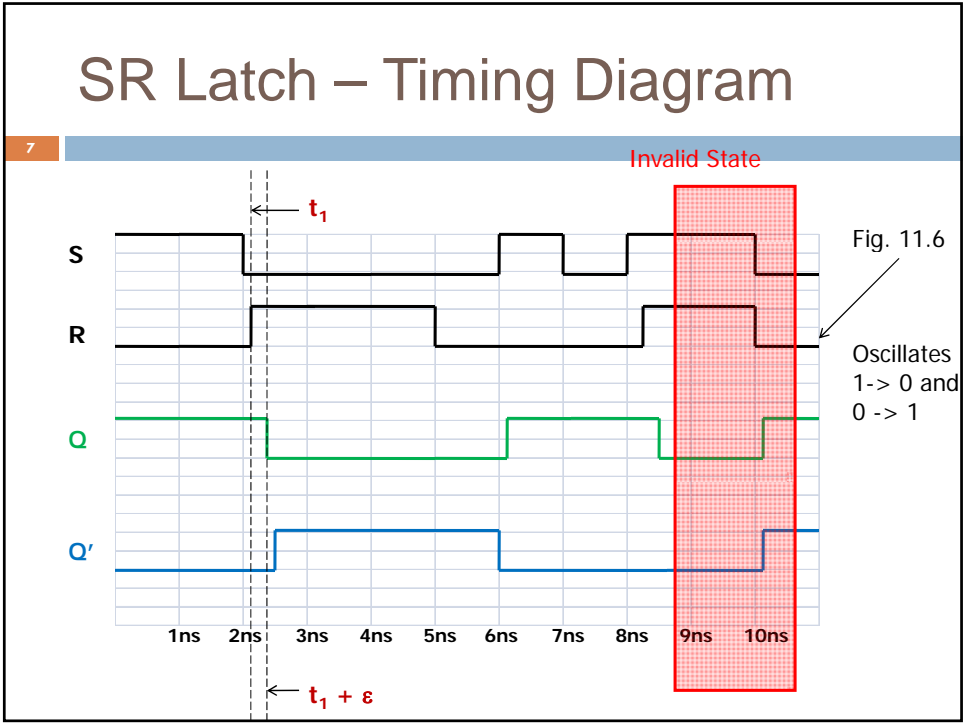

S'R' Latch


9

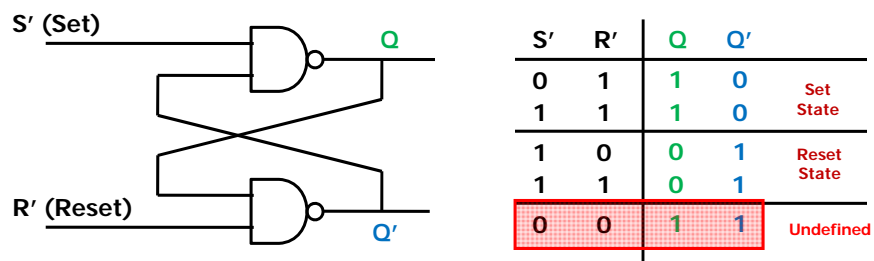- S'R' Latch is similar to SR, but built using NAND gates
- ▣ Set=0 and R=1 ⇒SETS the Q (1) output and RESETS Q' (0) (Write)
- ▣ Set=1 and R=0 ⇒RESETS the Q output (0) and SETS Q' (1) (Erase)
- ▣ Set=1 and R=1 ⇒Retains the states of Q and Q' (No change: Storage)
- ▣ Set=0 and R=0 ⇒invalid or forbidden state Q=Q'=0! (No use)



S'R' Latch – Timing Diagram


10

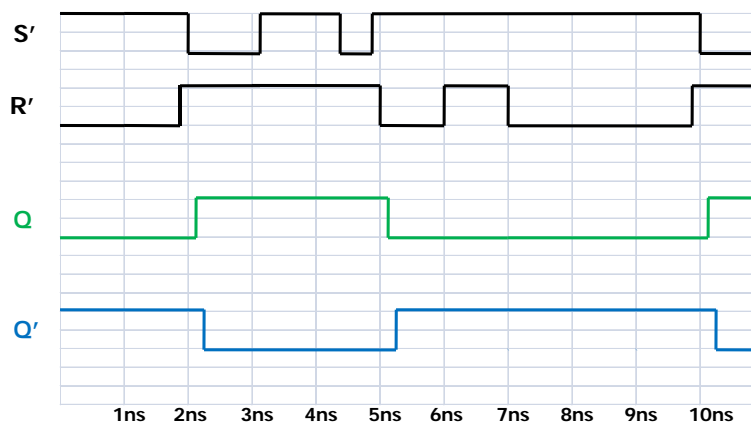

Clocked SR Latch


11

- Apply SR inputs through individual NAND gates with the other inputs coming from a **clock input (C)**
 - Will evaluate SR inputs and thus Latch only when $C=1$
 - When $C=0 \Rightarrow (C.S)'=1 \Rightarrow$ so $S'R'=11$ (No change)
 - When $C=1 \Rightarrow (C.S)'=S' \Rightarrow$ inputs to $S'R'$ latch
 - Due to clocked inputs $S'R'$ Latch becomes SR Latch
- A way to ensure timing of many latches in the system

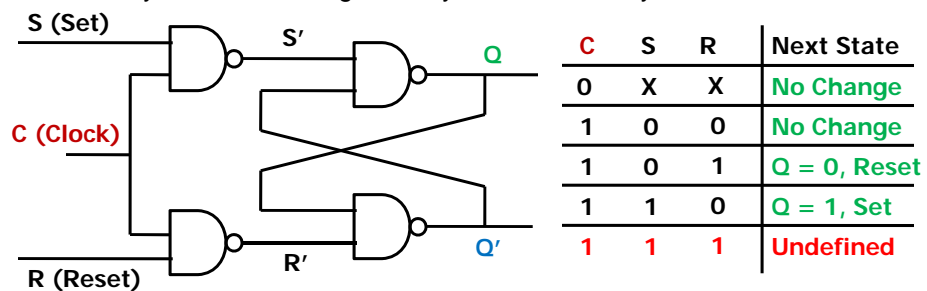

Clocked SR Latch – Timing Diagram


12

 

Gated D Latch

13

 - One way to eliminate the undesirable state in SR latch is to ensure that S and R are never equal to 1 at the same time



C	D	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


C	D	Next state (Q ⁺)
0	X	No Change
1	0	Q = 0, Reset
1	1	Q = 1, Set



$Q^+ = C'Q + CD$
(Characteristic Equation)

Gated D Latch – Timing Diagram

14

 

Flip-Flops

15

- Latches suffer from **transparency problem** as well as serious timing issues
 - If the clock has a relatively long pulse, the inputs (from other latches) **may change more than once causing the output to change**

- **The solution is to use Flip-Flops:** These are latches augmented with additional circuits to switch by a momentary change in the input control

Flip Flops

16



- FFs have a clock input and the output changes only in response to a rising or falling edge of the clock

- **Edge-Triggered:** Triggers only during a signal transition from 0 to 1 (or from 1 to 0) on the clock and disabled at all other times (even when $C = 1$)

- **A 2-stage master (recorder)-slave (reporter) FF with edge triggering**


Edge-Triggered D-Flip Flop

17

  


Rising Edge-Triggered D-Flip Flop

18

 

Falling Edge Triggered D-Flip Flop

19

 


Note that Output (Q) follows input (D) after each falling edge of the Clock (Ck) in the timing diagram

Important parameters: propagation delay, setup time, hold time


SR Flip Flop

20

 

Rising Edge Triggered SR Flip Flop

21

 


JK Flip-Flop (J = S, K = R)

22



$$Q^+ = JQ' + K'Q$$


(Characteristic Equation)

 

Rising Edge-Triggered JK FF

23

 
- In JK FF, J (S) = 1 and K (R) = 1 is allowed and causes the output to complement its value




T Flip Flop

24

 - T Flip Flop, called as Toggle FF is frequently used in building counters



 
$Q^+ = T \oplus Q$
(Characteristic Equation)



Asynchronous JK FF


25

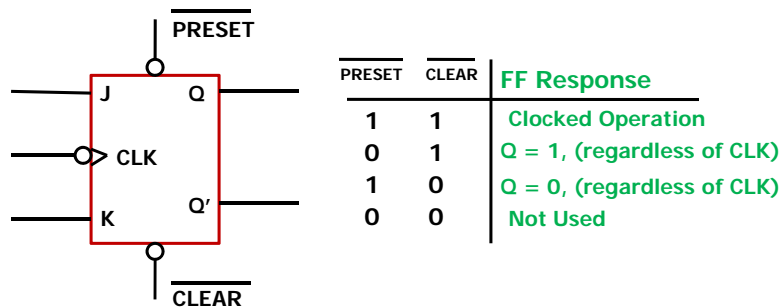- J, K are synchronous inputs
 - ▣ Effect on the output synchronous with CLK input
- In some JK FF, there maybe asynchronous inputs which operate independent of inputs and clock
 - ▣ Set the FF to 1/0 state at any time



Asynchronous JK FF

26

 

FF Summary

27

Flip-Flop Characteristic Table

JK Flip-Flop				SR Flip-Flop			
J	K	Q ⁺	Operation	S	R	Q ⁺	Operation
0	0	Q	No Change	0	0	Q	No Change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	Q'	Complement	1	1	?	Undefined

D Flip-Flop			T Flip-Flop		
D	Q ⁺	Operation	T	Q ⁺	Operation
0	0	Reset	0	Q	No Change
1	1	Set	1	Q'	Complement