

# EE 224: INTRODUCTION TO DIGITAL CIRCUITS & COMPUTER DESIGN

## Lecture 5: Sequential Logic - 2 Analysis of Clocked Sequential Systems

4/21/2010

Avinash Kodi, [kodi@ohio.edu](mailto:kodi@ohio.edu)

## Course Administration

2

- Hw 2 due on today Monday 4/26
- Hw 3 posted, due on Friday 4/30 by 1:00 PM  
(drop outside my office)
- Quiz 2 on Wednesday 4/28
- **Exam 1 on Monday 5/3 – syllabus next slide**

## Exam 1 - Syllabus

3

- Number System and Binary Arithmetic
- Boolean Algebra, Simplification and K-maps
- Combinational Logic (Adders, Muxes, Decoders, PLAs)
- Sequential Logic (Latches and Flip Flops)
- Analysis of Clocked Sequential Logic (Moore and Mealy machines)

## FF Summary

4

**Flip-Flop Characteristic Table**

JK Flip-Flop				SR Flip-Flop			
J	K	Q <sup>+</sup>	Operation	S	R	Q <sup>+</sup>	Operation
0	0	Q	No Change	0	0	Q	No Change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	Q'	Complement	1	1	?	Undefined

D Flip-Flop			T Flip-Flop		
D	Q <sup>+</sup>	Operation	T	Q <sup>+</sup>	Operation
0	0	Reset	0	Q	No Change
1	1	Set	1	Q'	Complement

## FF Transition Input Codes

5

- Using FF state tables we can derive the input conditions that will cause specific transitions in each FF output

- 4 possible transitions:
  - D & T FFs have well-defined input conditions in each case
  - J-K FF has 'Don't Care' (X) conditions
- Key to follow sequential logic circuit design examples (i.e. counters)

FF Outputs		FF Inputs		
Q(t)	Q(t+1)	T	D	J-K
0	→ 0	0	0	0-X
0	→ 1	1	1	1-X
1	→ 0	1	0	X-1
1	→ 1	0	1	X-0

## FF Excitation Table

6

Flip-Flop Excitation Table

JK Flip-Flop				SR Flip-Flop			
Q	Q <sup>+</sup>	J	K	Q	Q <sup>+</sup>	S	R
0	0	0	X	0	0	0	X
0	1	1	X	0	1	1	0
1	0	X	1	1	0	0	1
1	1	X	0	1	1	X	0

D Flip-Flop			T Flip-Flop		
Q	Q <sup>+</sup>	D	Q	Q <sup>+</sup>	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

## Analysis by Signal Tracing and Timing Charts

7

- **Analysis steps:**
  - Assume an initial state of FFs (all FFs reset to 0 unless specified)
  - For the input sequence, determine the circuit output(s) and FF inputs
  - Determine the new set of FF states after the next active clock edge
  - Determine the output(s) that corresponds to the new states

## Two Types of Clocked Sequential Circuits

8

- **Moore Machine:** If the output of a sequential circuit is a function of the **present state** only
- **Mealy Machine:** If the output of a sequential circuit is a function of both the **present state and the input**

## State Tables and Graphs

9

### State Table Construction


- ▣ **Step 1:** Determine the FF input equations and output equations from the circuit
- ▣ **Step 2:** Derive the next state equation for each FF from input equations from the circuit

D FF:  $Q^+ = D$   
 T FF:  $Q^+ = T \oplus Q$   
 SR FF:  $Q^+ = S + R'Q$   
 JK FF:  $Q^+ = JQ' + K'Q$

- ▣ **Step 3:** Plot a next state map for each FF
- ▣ **Step 4:** Combine the maps to form a state table


## Example of Moore's Machine (1/4)

10

 

## Example of Moore's Machine (2/4)

11

 Assume the initial value of  $A = 0$ ,  $B = 0$ ,  $Z = 0$ 

## Example of Moore's Machine (3/4)

12

- Step 1: FF input equations and output equations:
  - $Z = A \oplus B$      $D_A = X \oplus B'$      $D_B = X + A$
- Step 2: Next state equations for the FF are:
  - $A^+ = X \oplus B'$      $B^+ = X + A$
- Step 3: Corresponding K-maps for  $A^+$  and  $B^+$

	$X$	
	0	1
$AB$		
00	1	0
01	0	1
11	0	1
10	1	0


	$X$	
	0	1
$AB$		
00	0	1
01	0	1
11	1	1
10	1	1

## Example of Moore's Machine (4/4)

13


- Step 4: Combine the K-maps into transition table shown here from which states can be derived

AB	A+B+		Z	Present State	Next State		Present Output (Z)
	X = 0	X = 1			X = 0	X = 1	
00	10	01	0	S0	S3	S1	0
01	00	11	1	S1	S0	S2	1
11	01	11	0	S2	S1	S2	0
10	11	01	1	S3	S2	S1	1

 

## Example of Mealy Machine (1/4)

14

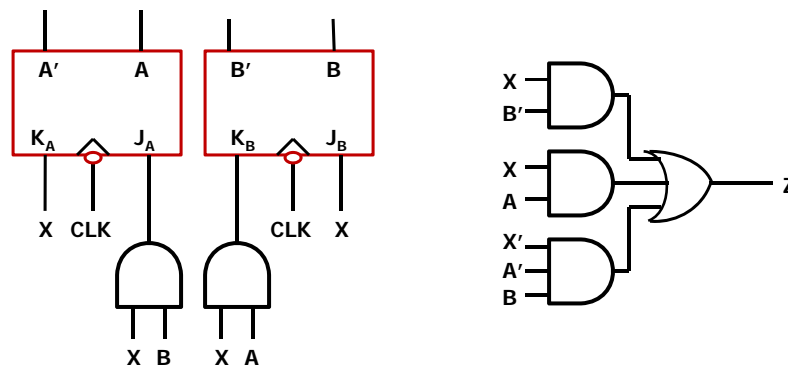


$$A^+ = J_A A' + K_A A = XBA' + X'A$$

$$B^+ = J_B B' + K_B B = XB' + (AX)'B = XB' + X'B + A'B$$

$$Z = X'A'B + XB' + XA$$

## Example of Mealy Machine (2/4)

15

 

## Example of Mealy Machine (3/4)

16

- Step 1: FF input equations and output equations:

$$J_A = XB, K_A = X \quad J_B = X, K_B = XA$$

- Step 2: Next state equations for the FF are:

$$\begin{aligned} A^+ &= XBA' + X'A \\ B^+ &= XB' + X'B + A'B \\ Z &= X'A'B + XB' + XA \end{aligned}$$

- Step 3: Corresponding K-maps for  $A^+$ ,  $B^+$  and  $Z$

		X	
		0	1
AB	00	0	0
	01	0	1
	11	1	0
	10	1	0

		X	
		0	1
AB	00	0	1
	01	1	1
	11	1	0
	10	0	1

		X	
		0	1
AB	00	0	1
	01	1	0
	11	0	1
	10	0	1




## Example of Mealy Machine (2/4)

17

- Step 4: Combine the K-maps into transition table shown here from which states can be derived

AB	A·B <sup>+</sup>		Z		Present State	Next State		Present Output (Z)	
	X = 0	X = 1	X = 0	X = 1		X = 0	X = 1	X = 0	X = 1
00	00	01	0	1	S0	S0	S1	0	1
01	01	11	1	0	S1	S1	S2	1	0
11	11	00	0	1	S2	S2	S0	0	1
10	10	01	0	1	S3	S3	S1	0	1

 

## Design of a Sequence Detector (1/3)

18


- Circuit examines a string of 0's and 1's applied to X input and generates an output  $Z = 1$  only when the prescribed sequence occurs with the assumption that X can only change between clock cycles. Design the circuit so that the input sequence ending in 101 will produce an output  $Z = 1$  coincident with the last 1. The circuit does not reset when a 1 occurs.

$X = 0\ 0\ 0\ 1\ 1\ 0\ 1\ 1\ 0\ 0\ 1\ 0\ 1\ 0\ 1\ 0\ 0$   
 $Z = 0\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 1\ 0\ 0$

- Is this a Mealy machine or Moore machine?

## Design of a Sequence Detector (2/3)

19

 

Present State	Next State		Present Output (Z)	
	X = 0	X = 1	X = 0	X = 1
S0	S0	S1	0	0
S1	S2	S1	0	0
S2	S0	S1	0	1

AB	A'B <sup>+</sup>		Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

## Design of a Sequence Detector (3/3)

20

	X	
AB	0	1
00	0	0
01	1	0
11	x	x
10	0	0

	X	
AB	0	1
00	0	1
01	0	1
11	x	x
10	0	1

	X	
AB	0	1
00	0	0
01	0	0
11	x	x
10	0	1


$$A^+ = X'B$$

$$B^+ = X$$

$$Z = XA$$

## How about Moore Machine?

21

 

Present State	Next State		Present Output (Z)
	X = 0	X = 1	
S0	S0	S1	0
S1	S2	S1	0
S2	S0	S3	0
S3	S2	S1	1

AB	A*B*		Z
	X = 0	X = 1	
00	00	01	0
01	11	01	0
11	00	10	0
10	11	01	1

## Complex Design - 1

22


- The output  $Z = 1$  if the input sequence ends in either 010 or 1001 and  $Z$  should be 0 otherwise. Here's a typical sequence

X = 0 0 1 0 1 0 0 1 0 0 0 1 0 0 1 1 0

Z = 0 0 0 1 0 1 0 1 1 0 0 0 1 0 1 0 0

## Solution - 1

23

 

State	Sequence Ends In
S0	Reset
S1	0 (but not 10)
S2	01
S3	10
S4	1 (but not 10)
S5	100

## Complex Design - 2


24

- A sequential circuit has one input ( $X$ ) and two outputs ( $Z1$  and  $Z2$ ). An output  $Z1 = 1$  occurs every time when the input sequence 100 is completed, provided that the sequence 010 has never occurred. An output  $Z2 = 1$  occurs every time the input sequence 010 is completed. Note that once  $Z2 = 1$  output has occurred,  $Z1 = 1$  can never occur but not vice versa. Find a mealy state graph and table.

$X$	=	1	0	0	1	1	0	0	1	0	1	0	1	0	0	1	0	1	1	0	1	0	0
$Z1$	=	0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$Z2$	=	0	0	0	0	0	0	0	0	1	0	1	0	1	0	0	1	0	0	0	0	1	0

## Solution - 2

25

 

## Complex Design - 3

26

- A sequential circuit has two inputs ( $X_1$  and  $X_2$ ) and one output  $Z$ . The output remembers the constant value unless one of the following input sequence occurs:
  - The input sequence  $X_1 X_2 = 01, 11$  causes the output to become 0
  - The input sequence  $X_1 X_2 = 10, 11$  causes the output to become 1
  - The input sequence  $X_1 X_2 = 10, 11$  causes the output to change value (toggle)

## Solution 3 (see text for complete solution)

27

Previous Input	Output (Z)	State Designation
00 or 11	0	S0
00 or 11	1	S1
01	0	S2
01	1	S3
10	0	S4
10	1	S5