

EE 224: INTRODUCTION TO DIGITAL CIRCUITS & COMPUTER DESIGN

Lecture 6: Sequential Logic – 3 Registers & Counters

05/10/2010

Avinash Kodi, kodi@ohio.edu

Introduction

2

- A Flip-Flop stores one bit of information – when a set of n Flip Flops is used to store n bits of data, we refer to them as REGISTER
- Common usage includes
 - ▣ Holding an output value from an arithmetic circuit (data registers)
 - ▣ Holding a count value in a counter circuit (Program Counter)
 - ▣ Keeping addresses for memory locations (Index Registers)
 - ▣ Many more
- A common clock signal is typically used for each FF in a register

Data Transfer



3

- Data transfer is a common function in computer systems
 - **Parallel** transfer: n-bits (full register contents) at a time
 - **Serial** transfer: 1-bit at a time (bit-by-bit)
- It is possible to convert transfer types in special registers:
 - **Parallel-to-serial**: load data into a register in one clock cycle (in parallel) but send out in series in n clock cycles
 - **Serial-to-parallel**: receive data in n clock cycles but can be accessed to all contents in parallel (n-bits)




Data Transfer

4



Serial Registers

  

Parallel Registers

   



Rotate Registers

  

Registers with Parallel Loading

5


 
 
- The simplest register consists of only FFs without external gates
 - The transfer of data is referred to as **loading the data**
 - Parallel loading if all the bits are loaded simultaneously with a common clock pulse



Registers with Parallel Loading

6

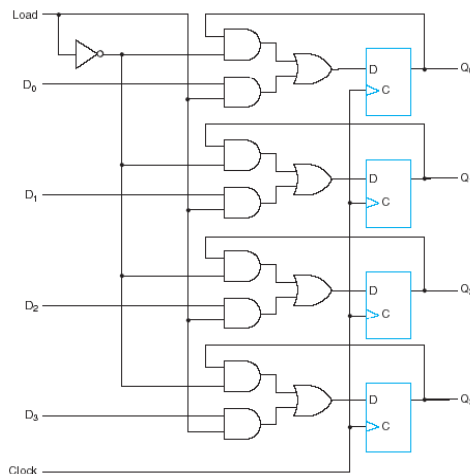  - The master clock generator supplies a continuous train of clock pulses. **When the register contents are to remain same the clock must be prevented from reaching the clock input.** Thus, a separate control signal is used to activate register loading.




A 4-bit register with a control load input

Shift Registers

7

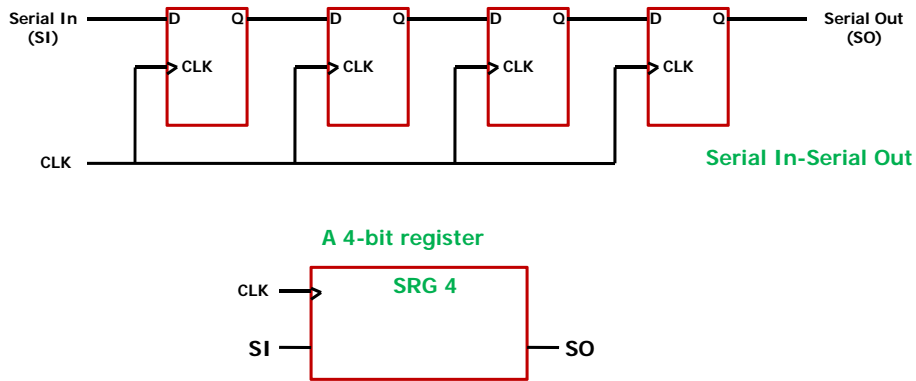
- Capable of shifting its storage bits laterally in one or both directions. They consist of a chain of flip-flops in cascade, with the output of one FF connected to input of the next FF. All FF receive a common clock pulse, which activates the shift from each stage to the next.



Serial Data Transfer

8

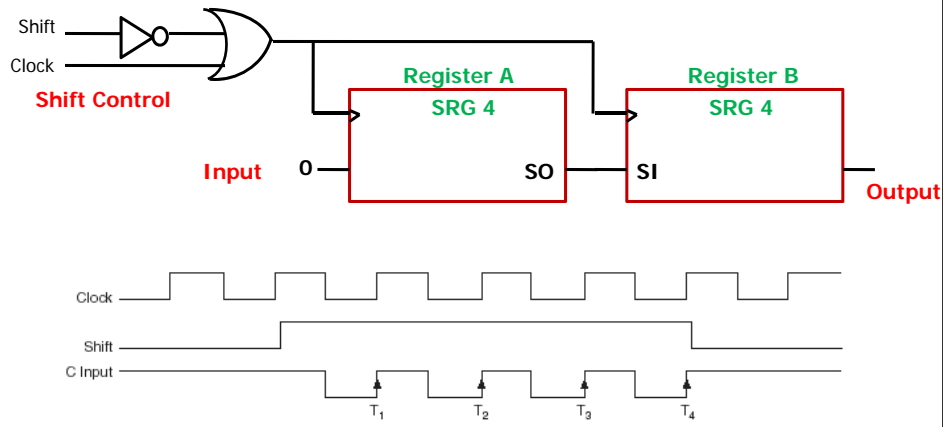
- A digital system is said to operate in a serial mode when information in the system is transferring one bit at a time



 Example

9


- Assume that binary content of registers A before the shift is 1011 and that of B is 0010 and SI of register A is 0




Timing pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	0 0 1 0
After T_1	0 1 0 1	1 0 0 1
After T_2	0 0 1 0	1 1 0 0
After T_3	0 0 0 1	0 1 1 0
After T_4	0 0 0 0	1 0 1 1

Registers with Serial Loading

10

 


A 4-bit register

 

Registers with Parallel Loading

11

 


(a) Logic diagram


Parallel In - Serial Out
Shift Register with Shift/Load Control

Bidirectional Shift Registers

12

 The data can be shifted either left or right. It can be implemented by using gating logic that enables the transfer direction of a data bit from one stage to the next stage (to the right or to the left), depending on the level of control signal (R/L').



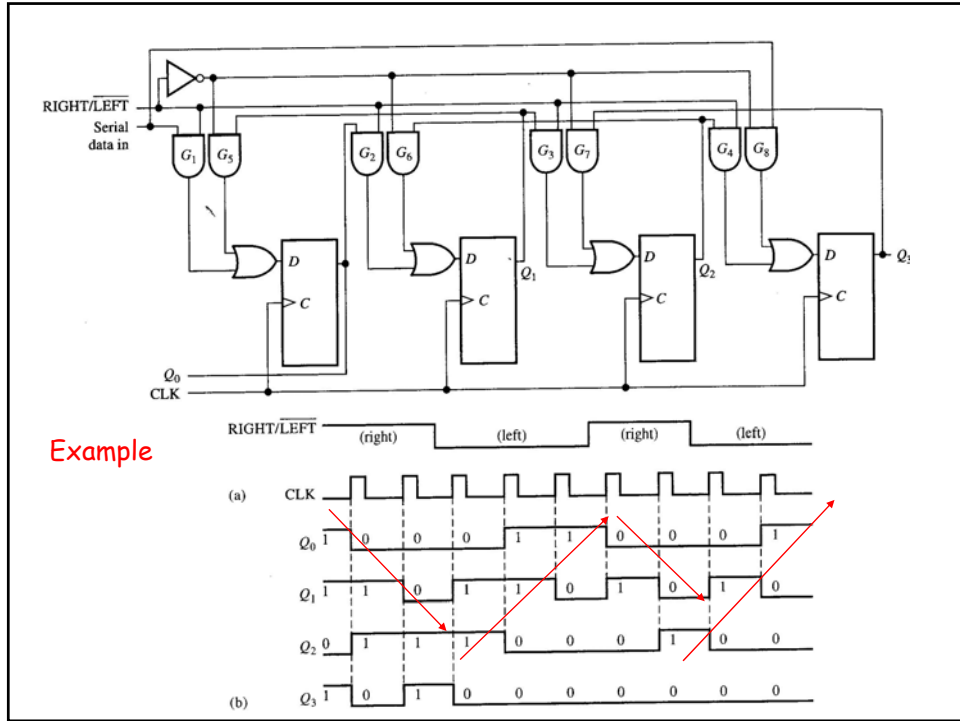

Flip Flop Summary

14

Flip-Flop Characteristic Table

JK Flip-Flop				SR Flip-Flop			
J	K	Q ⁺	Operation	S	R	Q ⁺	Operation
0	0	Q	No Change	0	0	Q	No Change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	Q'	Complement	1	1	?	Undefined

D Flip-Flop			T Flip-Flop		
D	Q ⁺	Operation	T	Q ⁺	Operation
0	0	Reset	0	Q	No Change
1	1	Set	1	Q'	Complement

FF Transition Input Codes

15

- Using FF state tables we can derive the input conditions that will cause specific transitions in each FF output

- 4 possible transitions:
 - D & T FFs have well-defined input conditions in each case
 - J-K FF has 'Don't Care' (X) conditions
- Key to follow sequential logic circuit design examples (i.e. counters)

FF Outputs		FF Inputs		
Q(t)	Q(t+1)	T	D	J-K
0	→ 0	0	0	0-X
0	→ 1	1	1	1-X
1	→ 0	1	0	X-1
1	→ 1	0	1	X-0

FF Excitation Table

16

Flip-Flop Excitation Table


JK Flip-Flop				SR Flip-Flop			
Q	Q ⁺	J	K	Q	Q ⁺	S	R
0	0	0	X	0	0	0	X
0	1	1	X	0	1	1	0
1	0	X	1	1	0	0	1
1	1	X	0	1	1	X	0

D Flip-Flop			T Flip-Flop		
Q	Q ⁺	D	Q	Q ⁺	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

Counters

17

- A register that goes through a prescribed sequence of states upon the application of input pulses.
 - The input pulses may be clock pulses or other sources, occurring at fixed or random intervals.
- An n-bit binary counter consists of n FF and can count in binary from 0 through $2^n - 1$. Counters can be of two types:
 - **Ripple counters**: the FF output transition serves as a source for triggering other FF.
 - **Synchronous counter**: the clock triggers all of the FFs
- Binary counters are most efficiently constructed with complementing **T** or **JK** FFs. They also can be designed with **D** FFs.

 

Synchronous Counters: Example 1


18

- The binary counters are constructed from **T** FFs
- All FFs are initially set to 0
- The sequence of **states** are:

000, 001, 010, 011, 100, 101, 110, 111

T Flip-Flop		
Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0



Present State			Next State			FF Inputs		
C	B	A	C ⁺	B ⁺	A ⁺	T _C	T _B	T _A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

T_A = 1
T_B = A
T_C = BA

Synchronous Counters: Example 1

19

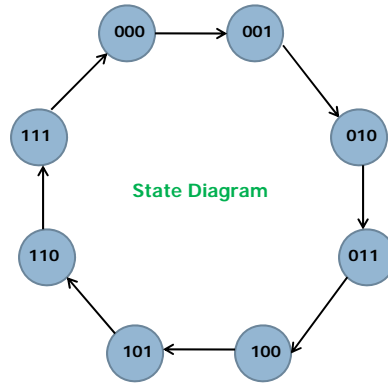 

C	B	A	C'	B'	A'	T _C	T _B	T _A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

State Table

Note that there is NO external input variable in this circuit (besides CLK signal) and FF outputs determine counter output


Synchronous Counter: Example 2

20

Use D FFs instead of T FF

000, 001, 010, 011, 100, 101, 110, 111

Present State			Next State			FF Inputs		
C	B	A	C'	B'	A'	D _C	D _B	D _A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

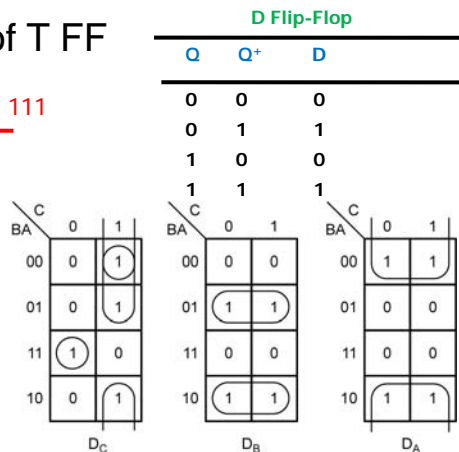

$$D_A = A' = A'$$

$$D_B = B' = BA' + B'A$$

$$D_C = C' = C'BA + CB' + CA'$$

$$= C'BA + C(B' + A') = C'BA + C(BA)'$$

Synchronous Counters: Example 2


21

$$D_A = A^+ = A'$$

$$D_B = B^+ = BA' + B'A = B \oplus A$$

$$D_C = C^+ = C'BA + CB' + CA' = C'BA + C(BA)' = C \oplus BA$$

Synchronous up-counter

 

Note that XOR of D FF output and input is equivalent to T FF (see previous notes on FF)

Example 3: Up and Down Counters

22

Up-down binary counter with D FFs, with U & D select bits for direction. Based on earlier examples, consider the modification:

$$D_A = A^+ = A \oplus (U + D)$$

$$D_B = B^+ = B \oplus (UA + DA')$$

$$D_C = C^+ = C \oplus (UBA + DB'A')$$

When U=0 and D=1 down-counter, (instead of A & BA we get A' & B'A')

$$D_A = A^+ = A \oplus 1 = A'$$

$$D_B = B^+ = B \oplus A'$$

$$D_C = C^+ = C \oplus B'A'$$

CBA	C'B'A'	
	U=1	D=1
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

When U=1 and D=0 up-counter. See earlier

When U=0 and D=0 no change. ABC preserved

When U=1 and D=1 is not to be used

Example 3: Up and Down Counters

23

Logic Circuit

CBA	C'B'A'	
	U=1	D=1
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

State Table

State Diagram

Example 4: Synchronous Counters

24

- Design a 4-bit synchronous counter using JK FF


JK Flip-Flop			
Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Example 4: Synchronous Counters

25

State Table and Flip-Flop Inputs for Binary Counter

Present state				Next state				Flip-flop inputs							
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃	Q ₂	Q ₁	Q ₀	J _{Q3}	K _{Q3}	J _{Q2}	K _{Q2}	J _{Q1}	K _{Q1}	J _{Q0}	K _{Q0}
0	0	0	0	0	0	0	1	0	x	0	x	0	x	1	x
0	0	0	1	0	0	1	0	0	x	0	x	1	x	x	1
0	0	1	0	0	0	1	1	0	x	0	x	x	0	1	x
0	0	1	1	0	1	0	0	0	x	1	x	x	1	x	1
0	1	0	0	0	1	0	1	0	x	x	0	0	x	1	x
0	1	0	1	0	1	1	0	0	x	x	0	1	x	x	1
0	1	1	0	0	1	1	1	0	x	x	0	x	0	1	x
0	1	1	1	1	0	0	0	1	x	x	1	x	1	x	1
1	0	0	0	1	0	0	1	x	0	0	x	0	x	1	x
1	0	0	1	1	0	1	0	x	0	0	x	1	x	x	1
1	0	1	0	1	1	0	0	x	0	1	x	x	1	x	1
1	0	1	1	1	1	0	0	x	0	1	x	x	1	x	1
1	1	0	0	1	1	0	1	x	0	x	0	0	x	1	x
1	1	0	1	1	1	1	0	x	0	x	0	1	x	x	1
1	1	1	0	1	1	1	1	x	0	x	0	x	0	1	x
1	1	1	1	0	0	0	0	x	1	x	1	x	1	x	1

 

Don't care states

It may be necessary to control the operation of the counter with a count-enable input.
 •When $EN=0$, all J and K inputs are equal to 0 and FFs remain in the same state.

Example 4: Synchronous Counters

26

$J_{Q3} = Q_0 Q_1 Q_2$

$K_{Q3} = Q_0 Q_1 Q_2$

$J_{Q1} = Q_0$

$K_{Q1} = Q_0$

$J_{Q2} = Q_0 Q_1$

$K_{Q2} = Q_0 Q_1$


$$\begin{aligned}
 J_{Q0} &= K_{Q0} = EN \\
 J_{Q1} &= K_{Q1} = Q_0 EN \\
 J_{Q2} &= K_{Q2} = Q_0 Q_1 EN \\
 J_{Q3} &= K_{Q3} = Q_0 Q_1 Q_2 EN
 \end{aligned}$$

The FF in the least significant position of a synchronous binary counter is complemented with a clock pulse transition.


Example 4: Synchronous Counters

27

Logic Circuit

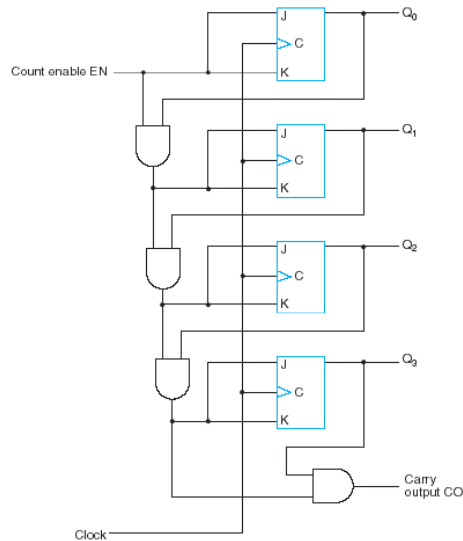

Symbol

 

Input Equations

$$J_{Q0} = K_{Q0} = EN$$

$$J_{Q1} = K_{Q1} = Q_0 EN$$

$$J_{Q2} = K_{Q2} = Q_0 Q_1 EN$$


$$J_{Q3} = K_{Q3} = Q_0 Q_1 Q_2 EN$$

Example 5: Arbitrary Counters with T FF

28

Counters for other sequences with T FFs.

Arbitrary Count Sequence.

 

If these numbers represent a given pattern (say on a screen), then such arbitrary counting sequences may be useful for 'display' purposes

Present State			Next State			FF Inputs		
C	B	A	C ⁺	B ⁺	A ⁺	T _C	T _B	T _A
0	0	0	1	0	0	1	0	0
0	0	1	-	-	-	X	X	X
0	1	0	0	1	1	0	0	1
0	1	1	0	0	0	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	-	-	-	X	X	X
1	1	0	-	-	-	X	X	X
1	1	1	0	1	0	1	0	1

Don't care states
Not completely specified

Example 5: Arbitrary Counters with T FF




29

T Flip-Flop

Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0




State Table

C	B	A	C ⁺	B ⁺	A ⁺	T _C	T _B	T _A
0	0	0	1	0	0	1	0	0
0	0	1	-	-	-	X	X	X
0	1	0	0	1	1	0	0	1
0	1	1	0	0	0	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	-	-	-	X	X	X
1	1	0	-	-	-	X	X	X
1	1	1	0	1	0	1	0	1

   

Example 5: Arbitrary Counters with T FF

30

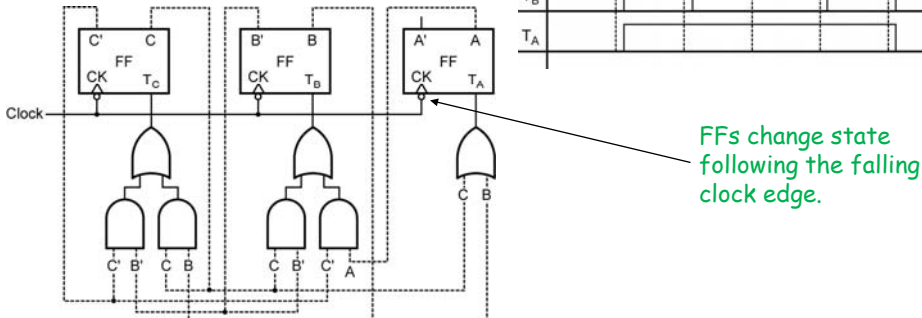  

Example 6: Arbitrary Counters with JK FF

31

State Table and Flip-Flop Inputs for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	1	0	0	1	x	x	1	0	x
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	1	1	0	x	0	1	x	x	1
1	1	0	0	0	0	x	1	x	1	0	x

Input Equations

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$

$$J_C = \overline{B} \quad K_C = 1$$

State Diagram

