

---

# EE 3613: Computer Organization

## Arithmetic for Computers – I

### Number Representation & ALU

Avinash Karanth

Department of Electrical Engineering & Computer Science

Ohio University, Athens, Ohio 45701

E-mail: [karanth@ohio.edu](mailto:karanth@ohio.edu)

Website: <http://oucsace.cs.ohiou.edu/~avinashk/classes/ee461a/ee461a.htm>

Acknowledgement: Srinivasan Ramasubramanian, Mary J. Irwin, PSU

1

---


## Course Administration

- Get started with Qt-SPIM ☺
- All lecture slides (including ISA) are posted
- Assignment 2 is posted – split into two parts
  - Part A is due next Friday, Sept 18
  - Part B is due the following Friday, Sept 25

2
 
## Arithmetic

- Where we have been
  - Performance (seconds, cycles, instructions)
- Abstractions
  - Instruction Set Architecture
  - Assembly Language and Machine Language (SPIM)
- What's up ahead?
  - Implementing the architecture (Chapter 3)



3

## Numbers

- Bits are just bits (no inherent meaning)
  - Conventions define relationship between bits and numbers
- Binary numbers (base 2)
  - 0000 0001 0010 0011 0100 0101 0110 0111 1000 1000
  - Decimal  $0 \dots 2^n - 1$
- Of course it gets more complicated
  - Numbers are finite (overflow)
  - Fractions and real numbers
  - Negative numbers
- How do we represent negative numbers?
  - i.e. which bit pattern will represent which numbers?

4

## Possible Representations

Code	Signed Magnitude	One's Complement	Two's Complement
000	+0	+0	0
001	+1	+1	+1
010	+2	+2	+2
011	+3	+3	+3
100	-0	-3	-4
101	-1	-2	-3
110	-2	-1	-2
111	-3	-0	-1

- Issues: balance, number of zeros, ease of operation
- Which one is best? Why?

5

## Number Representation

- **32 bit signed numbers**
  - 0000 0000 0000 0000 0000 0000 0000 0000 = 0
  - 0000 0000 0000 0000 0000 0000 0000 0001 = +1
  - 0000 0000 0000 0000 0000 0000 0000 0010 = +2
  - .....
  - 0111 1111 1111 1111 1111 1111 1111 1110 = +2, 147,483, 646
  - 0111 1111 1111 1111 1111 1111 1111 1111 = +2, 147,483, 647
  - 1000 0000 0000 0000 0000 0000 0000 0000 = -2, 147, 483, 648
  - 1000 0000 0000 0000 0000 0000 0000 0001 = -2, 147, 483, 647
  - 1000 0000 0000 0000 0000 0000 0000 0010 = -2, 147, 483, 646
  - .....
  - 1111 1111 1111 1111 1111 1111 1111 1110 = -2
  - 1111 1111 1111 1111 1111 1111 1111 1111 = -1

6

## Two's Complement Operations

- Representing positive and negative numbers
  - $(b_{31} \times -2^{31}) + (b_{30} \times 2^{30}) + (b_{29} \times 2^{29}) + \dots + (b_1 \times 2^1) + (b_0 \times 2^0)$
- Negating a two's complement number: invert all bits and add 1
  - Remember: "negate" and "invert" are quite different
- Converting n bits numbers into numbers with more than n bits
  - MIPS 16 bit immediate gets converted to 32 bits for arithmetic
  - Copy the most significant bit (sign bit) into the other bits
  - 0010 → 0000 0010
  - 1010 → 1111 1010

7

## 2's Complement Binary Representation

- Negate

$$-2^3 =$$

$$-(2^3 - 1) =$$

1011

and add a 1

1010

complement all the bits

- Note: negate and invert are different!

$$2^3 - 1 =$$

2'sc binary	decimal
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7

8

## Addition and Subtraction

- Just like in high school (carry/borrow 1s)

- Add  $6_{10}$  to  $7_{10}$

$$\begin{array}{r} 0111 \\ 0110+ \\ \hline 1101 \end{array}$$

- Subtract  $6_{10}$  from  $7_{10}$

$$\begin{array}{r} 0111 \\ 0110- \\ \hline 0001 \end{array}$$

- Subtract  $6_{10}$  from  $7_{10}$  (in two's complement)

$$\begin{array}{r} 0111 \\ 1010+ \\ \hline 0001 \end{array}$$

- Overflow (result too large for finite computer word)
  - Eg. Adding two n-bit numbers does not yield an n-bit numbers

9

## Adder: Boolean Algebra

A	B	Carry In	Carry Out	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Carry Out =  $A \cdot B + B \cdot C + A \cdot C$
- SUM =  $A \cdot B \cdot C + A' \cdot B' \cdot C + A' \cdot B \cdot C' + A \cdot B' \cdot C'$

10

# Review: Boolean Algebra and Gates

- Problem: Consider a logic function with 3 inputs: A, B and C
- **Output D** is true if atleast one input is true
- **Output E** is true if exactly two inputs are true
- **Output F** is true if all three inputs are true
  - Show the truth table for these three functions
  - Show the Boolean equations for these three functions
  - Show an implementation consisting of inverters, OR and AND gates

A	B	C	D	E	F
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

D =




E =

F =

11
   
# One-bit Adder


- Takes three input bits and generates two output bits
- Multiple bits can be cascaded



12
 
## Detecting Overflow

- Overflow: the result is too large to represent in 32 bits
- Overflow occurs when
  - adding two positives yields a negative
  - or, adding two negatives gives a positive
  - or, subtract a negative from a positive gives a negative
  - or, subtract a positive from a negative gives a positive
- On your own: **Prove** you can detect overflow by:
  - Carry into MSB xor Carry out of MSB, ex for 4 bit signed numbers



13


## Effects of Overflow

- An **exception (interrupt)** occurs
  - Control jumps to predefined address for exception
  - Interrupted address is saved for possible resumption
- Details based on software system/language
- Don't always want to detect overflow
  - New MIPS instructions: addu, addiu, subu

14
 
## An ALU (Arithmetic Logic Unit)

- Let's build an ALU to support **and** and **or** instructions
  - We will build a 1-bit ALU and use 32 of them




Op	A	B	Result

- Possible Implementation (sum-of-products)
  - Not easy to decide the "best" way to build something

15
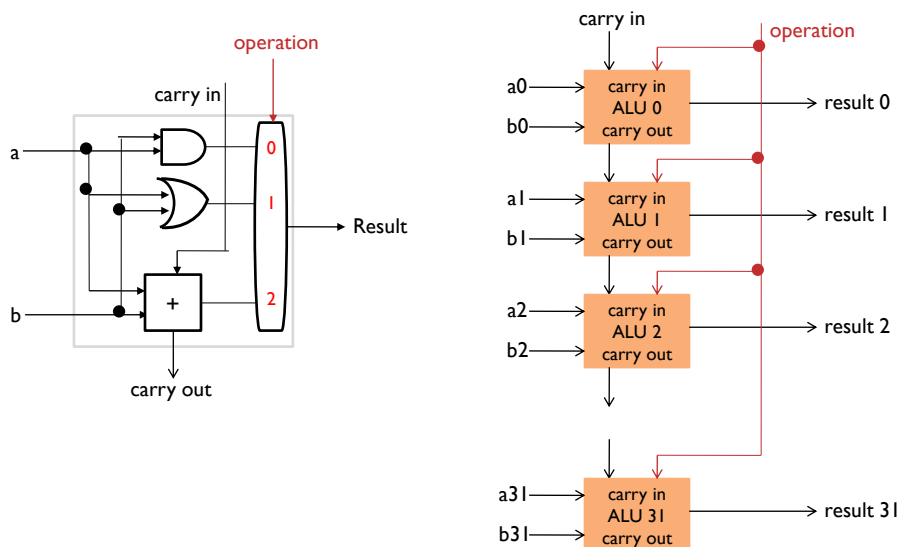
## Building a 32-bit ALU (AND, OR and ADD)




16


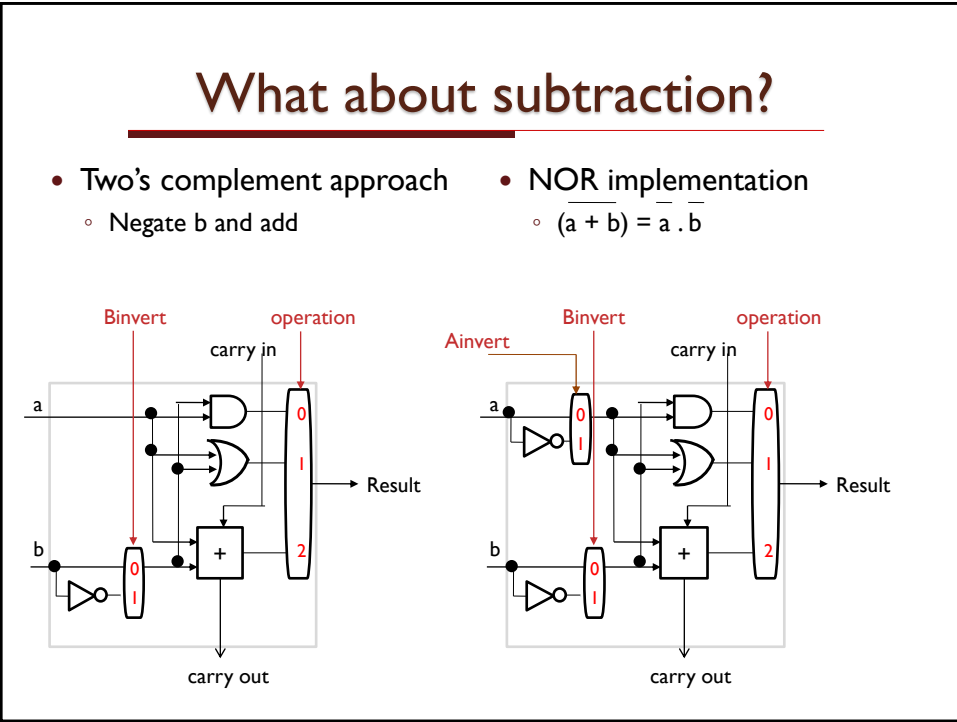
# What about subtraction?


- Two's complement approach
  - Negate b and add
- NOR implementation
  - $(a + b) = \overline{\overline{a} \cdot \overline{b}}$



17

# Supporting slt and Overflow Detection


- Can you figure out the idea?

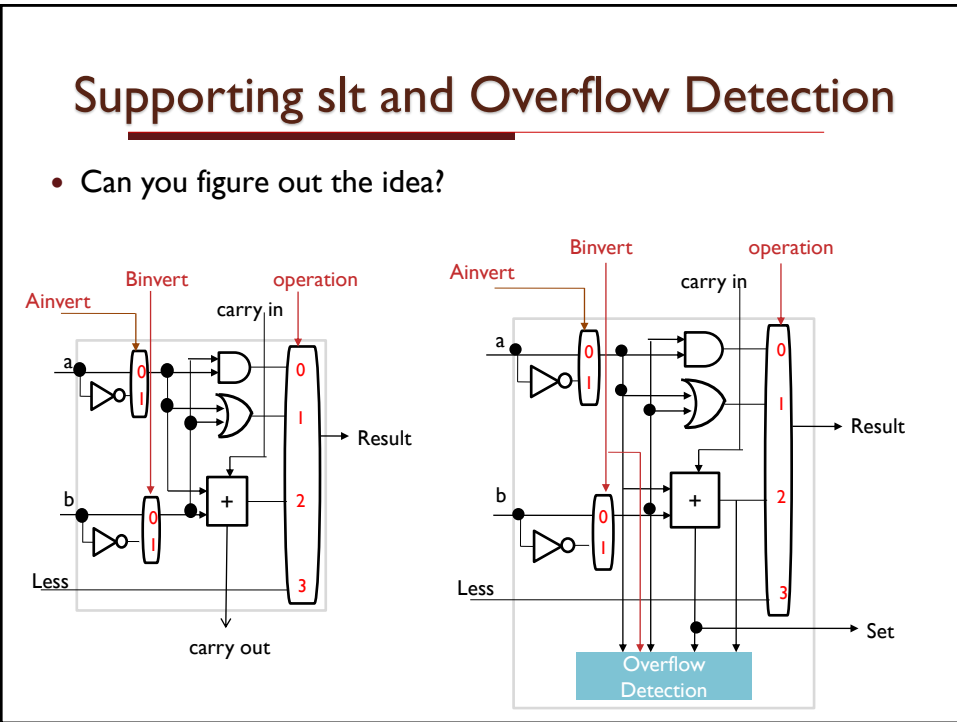

18
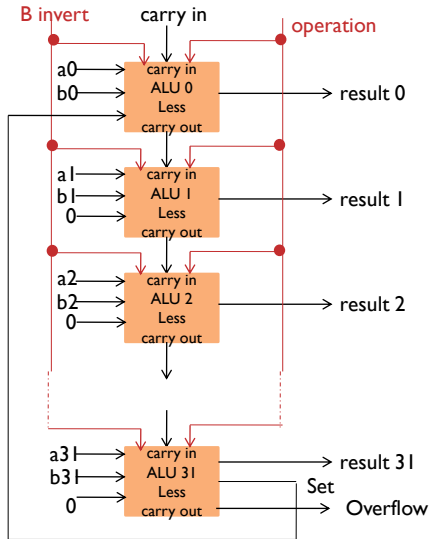
## A 32-Bit ALU


- A ripple carry ALU
- Two bits to decide
  - ADD/SUB
  - AND
  - OR
  - LESS
- A carry-in bit
  - Combine with *Binvert* to obtain *Bnegate*
- Bit 31 generates set and overflow
- How to implement **branch instructions?**



19
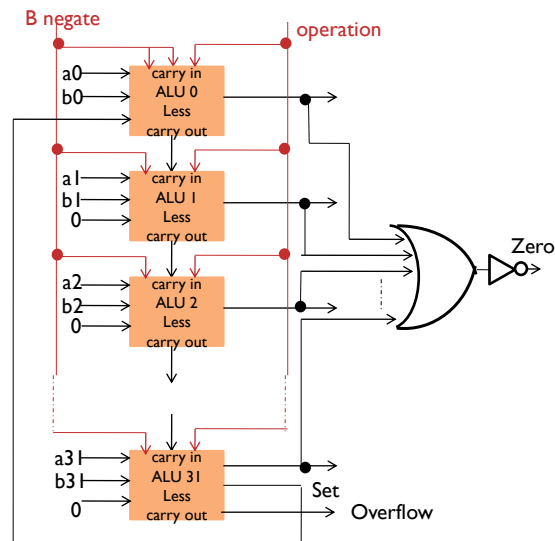
## Test for Equality

- Notice the control lines
  - 000 = AND
  - 001 = OR
  - 010 = ADD
  - 110 = SUBTRACT
  - 111 = SLT



20

## Conclusions

---

- We can build ALU to support the **MIPS instruction set**
  - **Key Idea:** Use multiplexor to select the output we want
  - Efficiently perform subtraction using two's complement
  - Replicate 1-bit ALU to produce a 32-bit ALU
- Important points about hardware
  - All of the gates are always working
  - The speed of the gate is affected by the number of inputs to the gate
  - The speed of a circuit is affected by the number of gates in series (on the critical path" or the "deepest level of logic")