
EE 3613: Computer Organization

Chapter 4: The Processor: Datapath & Control - 3

Avinash Karanth

Department of Electrical Engineering & Computer Science

Ohio University, Athens, Ohio 45701

E-mail: karanth@ohio.edu

Website: <http://oucsace.cs.ohiou.edu/~avinashk/ee461a.htm>

Acknowledgement: Srinivasan Ramasubramanian, UofA, Mary J. Irwin, PSU

1

Course Administration

- All lecture notes (including Verilog tutorial) available
- Homework 3 will be made available later today; this is due in two parts:
 - Part A is due this Friday, Oct 16
 - Part B (Verilog) is due on Monday Oct 26

2


Datapath and Control

- We will design a simplified MIPS processor
- The instructions supported are
 - Memory-reference instructions: **lw, sw**
 - Arithmetic-logical instructions: **add, sub, and, or, slt**
 - Control-flow instructions: **beq, j**
- Generic Implementation
 - Use the program counter (PC) to supply the instruction address and fetch the instruction from memory (and update the PC)
 - Decode the instruction (and read the registers)
 - Execute the instruction
- All instructions (except j) use the ALU after reading the registers
 - How? Memory-reference ? Arithmetic ? Control-flow ?

3

Clocking Methodologies

 - The clocking methodology defines when signals can be **read** and when they can be **written**
 - **An edge triggered methodology**
- Typical execution
 - **Read** contents of state elements
 - **Send** values through combinational logic
 - **Write** results to one or more state elements





- Assumes that state elements are written on every clock cycle; if not, need explicit write control signal
 - Writes occur only when **both** the write control is asserted and clock edge occurs

4


What blocks do we need?

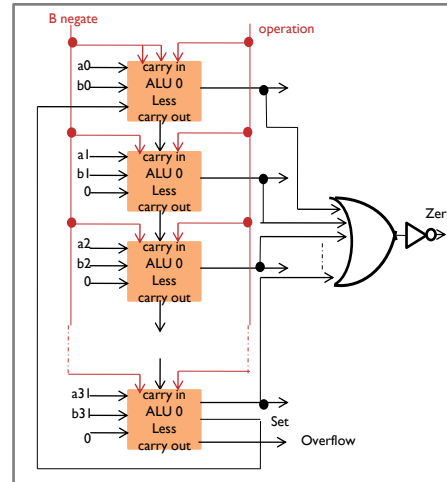 - We need an **ALU** – already designed a 4 function (ADD/SUB, OR,AND, SLT) and **BRANCH**



5


A Static Memory Cell

 

- Tri-state Logic:** The output of a gate can be in one of **three** states – one, zero or not connected

6



4-bit Register

 

7


What more blocks do we need?

  - We need **memory** to store instructions and data
 - Instruction memory takes address and supplies instructions
 - Data memory takes address and supply data (eg. load)
 - Data memory takes address and data and write into memory



8

Sample 4 x 3 Memory

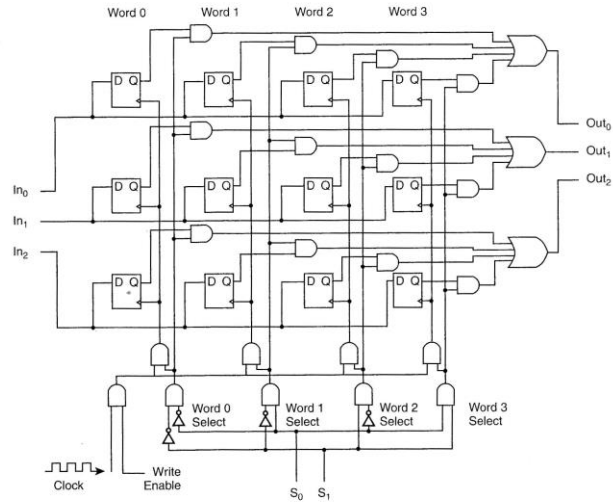


<http://www.sci.brooklyn.cuny.edu/~jones/cisc3310/Null%20&%20Lobur%20Figures.htm>

9

Other Blocks?

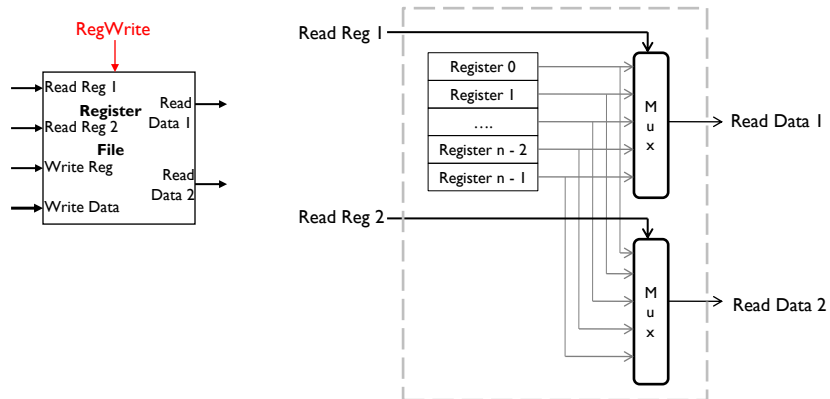
- We need **register file** to include 32 registers
 - 2 port read for a register file



10

Other Blocks?

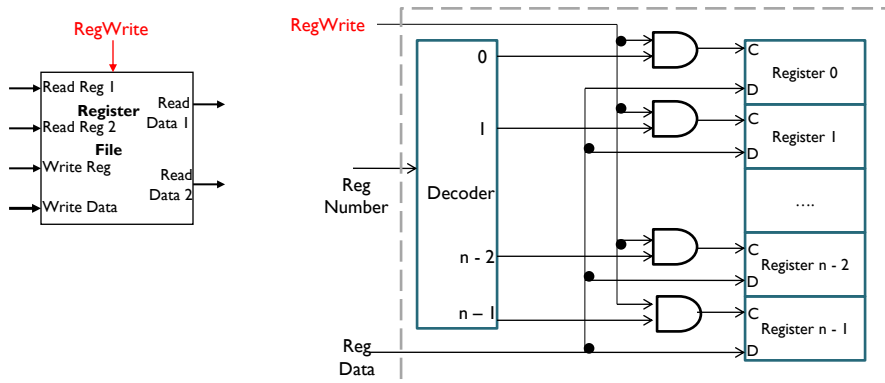- We need register file to include 32 registers
 - Implement write port with **write** control



11


Any other blocks?

- PC (program counter)
- Add support for immediate class of instructions
- Add support for J, JR, JAL

12

Fetching Instructions

 - Fetching instructions involves
 - reading the instruction from the **Instruction Memory**
 - **updating the PC** to hold the address of the next instruction




- PC is updated every cycle, so it does not need an explicit write control signal
- Instruction memory is read every cycle, so it doesn't need an explicit read control signal

13

Decoding Instructions

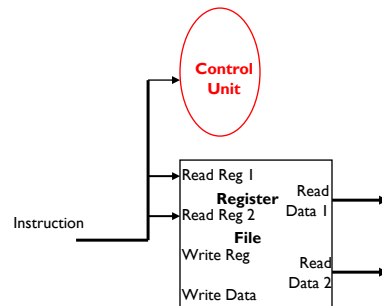- Decoding instructions involves
 - sending the fetched instruction's **opcode** and **function field bits** to the control unit




- reading two values from the **Register File**
 - Register File addresses are contained in the instruction


14

Executing R Format Operations

 - R format operations (**add**, **sub**, **slt**, **and**, **or**)



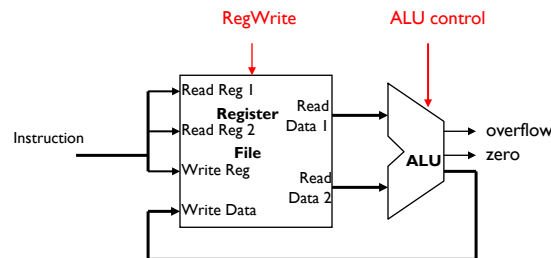- perform the (**op** and **funct**) operation on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)




- The Register File is not written every cycle (e.g. **sw**), so we need an explicit write control signal for the Register File

15

Executing Load Operation

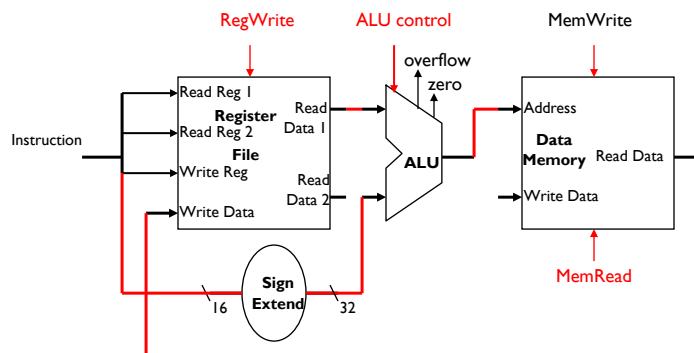
- Load and store operations involves
 - compute memory address by adding the base register (read from the **Register File** during decode) to the 16-bit signed-extended offset field in the instruction
 - load** value, read from the Data Memory, written to the Register File



16

Executing Store Operation

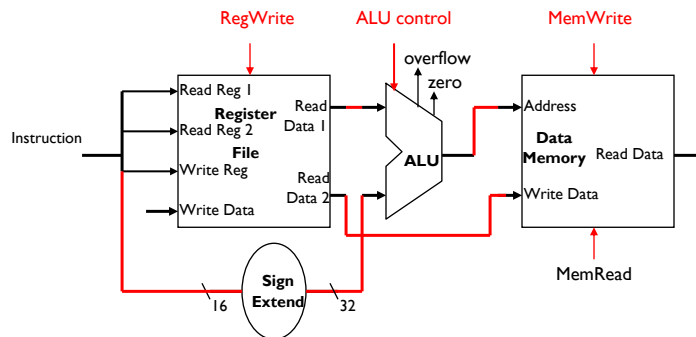
- Load and store operations involves
 - compute memory address by adding the base register (read from the **Register File** during decode) to the 16-bit signed-extended offset field in the instruction
 - **store** value (read from the Register File during decode) written to the Data Memory



17

Executing Branch Operations

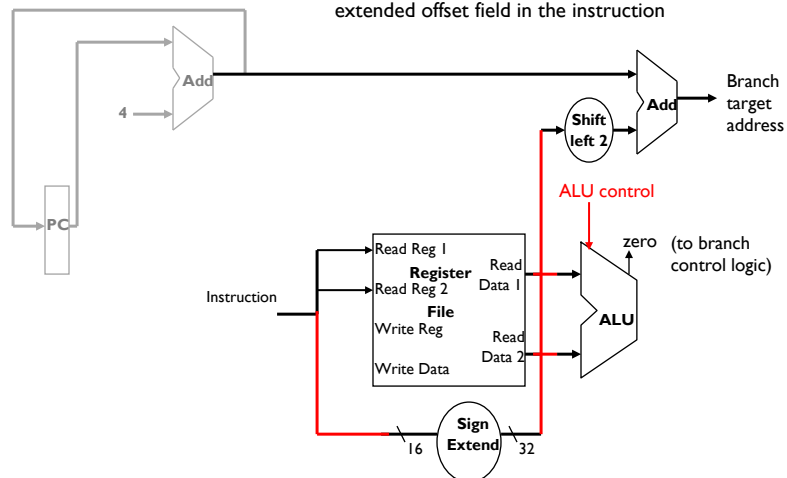
- Branch operations involves
 - compare the operands read from the Register File during decode for equality (**zero** ALU output) compute the branch target address by adding the updated PC to the 16-bit signed-extended offset field in the instruction



18

Executing Jump Operations

 - Jump operation involves
 - replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits




19

Creating a Single Datapath from the Parts

- Assemble the datapath segments and add control lines and multiplexors as needed
- **Single cycle** design – fetch, decode, and execute each instructions in one cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (Eg. separate **Instruction Memory** and **Data Memory**, several adders)
 - **multiplexors** needed at the input of shared elements with the control lines to do the selection
 - write signals to control writing to the **Register File** and **Data Memory**
- **Cycle time** is determined by length of the longest path

20

Fetch, R, and Memory Access Portions

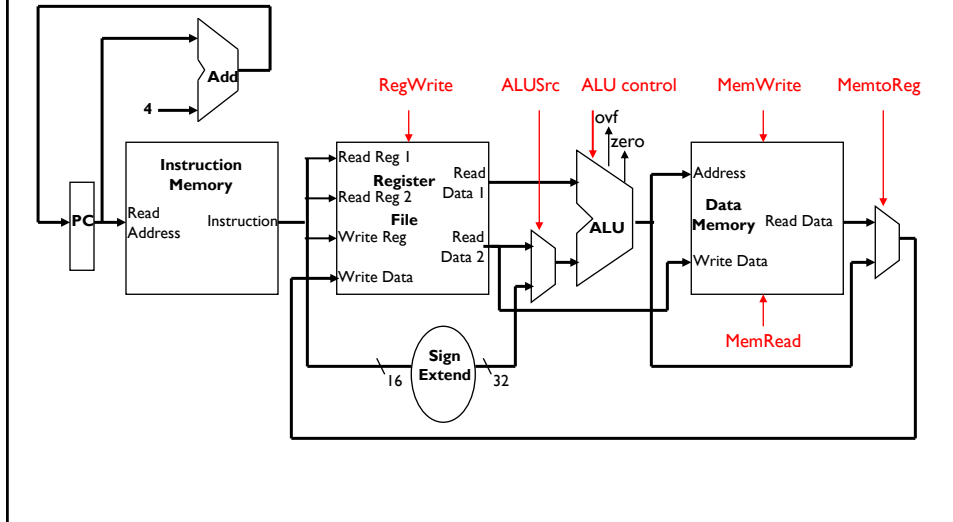


21

Adding the Control

- Selecting the operations to perform (ALU, Register File, Memory read/write)
 - Select the registers to be read (always two)
 - Select the 2nd ALU input
 - Select the operation to be performed
 - Select the data memory to be written
- Controlling the flow of data (multiplexor inputs)

22

Adding the Control

 


- Observations

- **op** field always in bits 31-26
- address of registers to be read are always specified by the **rs** field (bits 25-21) and **rt** field (bits 20-16); for lw and sw, **rs** is the base register
- addr. of register to be written is in one of two places – in **rt** (bits 20-16) for lw; in **rd** (bits 15-11) for R-type instructions
- offset for beq, lw, and sw always in bits 15-0


23

Single Cycle Datapath with Control Unit

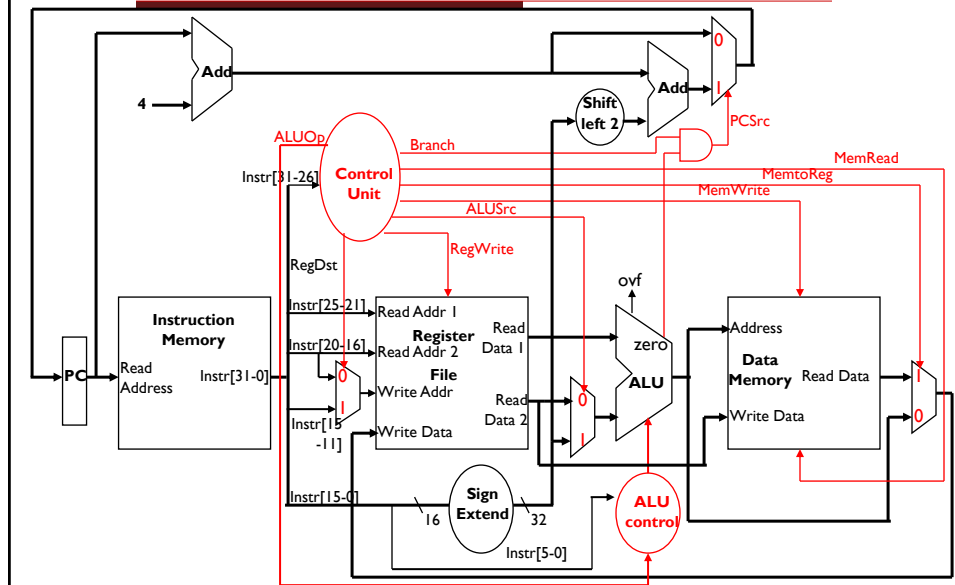


24

Load Word Instruction Data/Control Flow

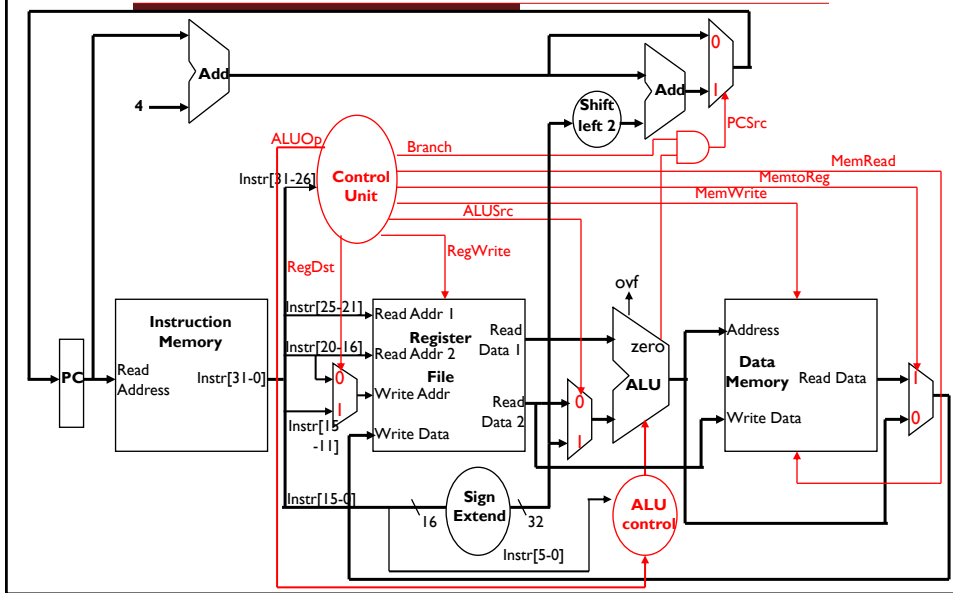


25

Branch Instruction Data/Control Flow

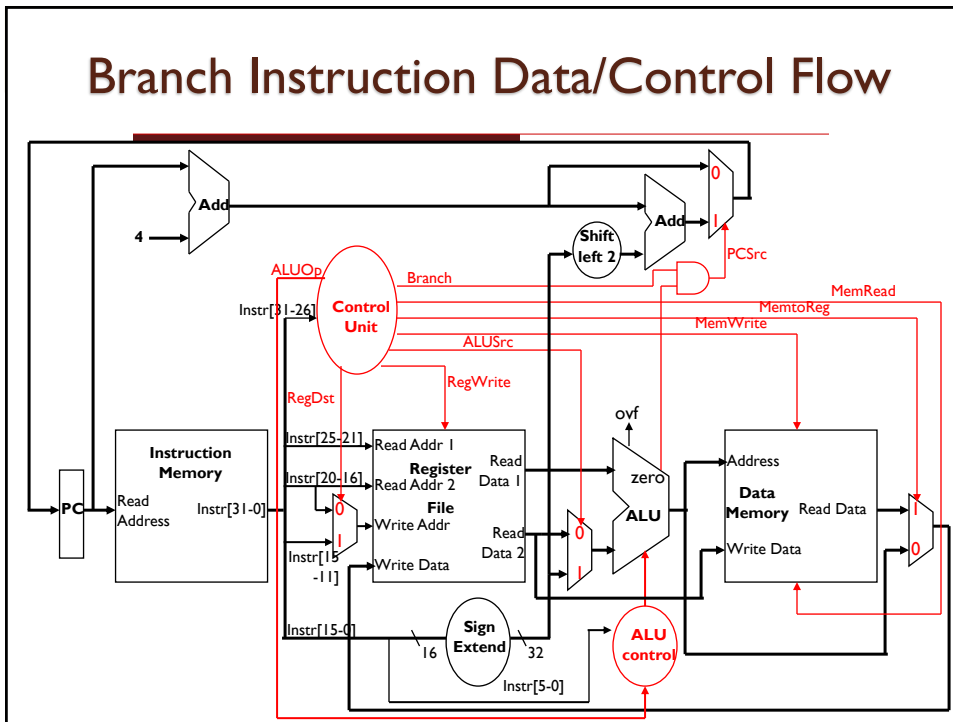

26

 

27